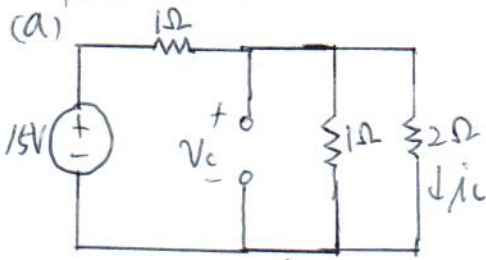


# # 1 Solution.


초기조건  $t=0^-$



$$V_c(0^-) = \frac{\frac{2}{2+1}}{\frac{2}{2+1} + 1} \times 15 = 6V \quad V_c(0^-) = V_c(0^+) = 6V$$

$$i_L(0^-) = \frac{6}{2} = 3A \quad i_L(0^-) = i_L(0^+) = 3A$$

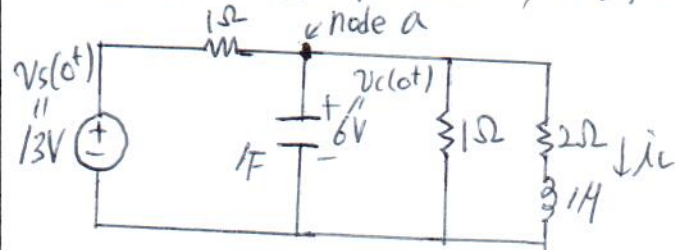$t=0^+$   $V_s = 13 \cos 2t$ ,  $V_s(0) = 13V$



node a에 KCL

$$\frac{V_c(0^+) - V_s(0^+)}{1} + i_L + C \left. \frac{dV_c}{dt} \right|_{0^+} + \frac{V_c(0^+)}{1} = 0$$


$$\frac{6-13}{1} + 3 + 1 \left. \frac{dV_c}{dt} \right|_{0^+} + 6 = 0$$

$$\therefore \left. \frac{dV_c}{dt} \right|_{0^+} = -2$$

$$V_c(0^+) = L \left. \frac{di_L}{dt} \right|_{0^+} + 2i_L(0^+) \text{ 이므로}$$

$$\therefore \left. \frac{di_L}{dt} \right|_{0^+} = 0$$

(b)  $t > 0^+$

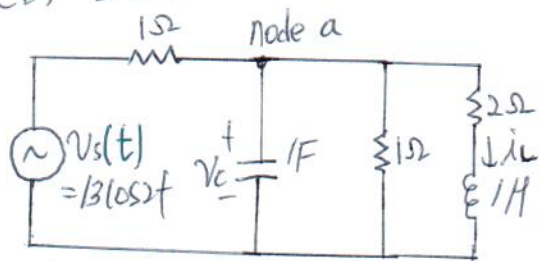

다시 node a 에서 KCL

$$\frac{v_c - v_s}{1} + i_L + C \frac{dv_c}{dt} + \frac{v_c}{1} = 0 \quad \dots (1)$$

$$v_c = L \frac{di_L}{dt} + 2i_L \quad \dots (2)$$

(1)식에 (2) 대입

$$\left( \frac{di_L}{dt} + 2i_L - v_s \right) + i_L + \frac{d}{dt} \left( \frac{di_L}{dt} + 2i_L \right) + \frac{di_L}{dt} + 2i_L = 0$$

$$\therefore \frac{d^2 i_L}{dt^2} + 4 \frac{di_L}{dt} + 5i_L = 13 \cos 2t$$

(c)  $i_L(t)$

$i_L(t) = i_{Lh} + i_{Lp}$  로 구성

$i_{Lh} = k e^{st}$  라 하자

$$\frac{d^2 i_{Lh}}{dt^2} + 4 \frac{di_{Lh}}{dt} + 5i_{Lh} = 0 \rightarrow s^2 + 4s + 5 = 0$$

특성방정식의 해는  $s = -2 \pm j$

$$i_{Lh} = e^{-2t} (k_1 \cos t + k_2 \sin t)$$

$i_{Lp}$

$$\frac{d^2 i_{Lp}}{dt^2} + 4 \frac{di_{Lp}}{dt} + 5i_{Lp} = 13 \cos 2t$$

$$\left. \begin{aligned} i_{Lp} \text{의 꼴은 } i_{Lp} &= A \cos 2t + B \sin 2t \\ i_{Lp}' &= -2A \sin 2t + 2B \cos 2t \\ i_{Lp}'' &= -4A \cos 2t - 4B \sin 2t \end{aligned} \right\} \text{를 위식에 대입}$$

$$(-4A \cos 2t - 4B \sin 2t) + 4(-2A \sin 2t + 2B \cos 2t) + 5(A \cos 2t + B \sin 2t) = 13 \cos 2t$$

$$(A \cos 2t + 8B \cos 2t) + (B \sin 2t - 8A \sin 2t) = 13 \cos 2t$$

$$A + 8B = 13, \quad B - 8A = 0$$

$$\therefore A = \frac{1}{5}, \quad B = \frac{8}{5}$$

$$i_L = \frac{1}{5} \cos 2t + \frac{8}{5} \sin 2t$$

$$i_L(t) = i_{Lh} + i_{Lp} = e^{-2t} (k_1 \cos t + k_2 \sin t) + \frac{1}{5} \cos 2t + \frac{8}{5} \sin 2t$$

$$i_L(0) = 3 = k_1 + \frac{1}{5}$$

$$\therefore k_1 = \frac{14}{5}$$

$$i_L'(t) = -2k_1 \cos t \cdot e^{-2t} - k_1 \sin t \cdot e^{-2t} - 2k_2 \sin t \cdot e^{-2t} + k_2 \cos t \cdot e^{-2t} - \frac{2}{5} \sin 2t + \frac{16}{5} \cos 2t$$

$$i_L'(0) = 0 = -2k_1 + k_2 + \frac{16}{5}$$


$$\therefore k_2 = \frac{12}{5}$$

$$\therefore i_L(t) = e^{-2t} \left( \frac{14}{5} \cos t + \frac{12}{5} \sin t \right) + \frac{1}{5} \cos 2t + \frac{8}{5} \sin 2t$$

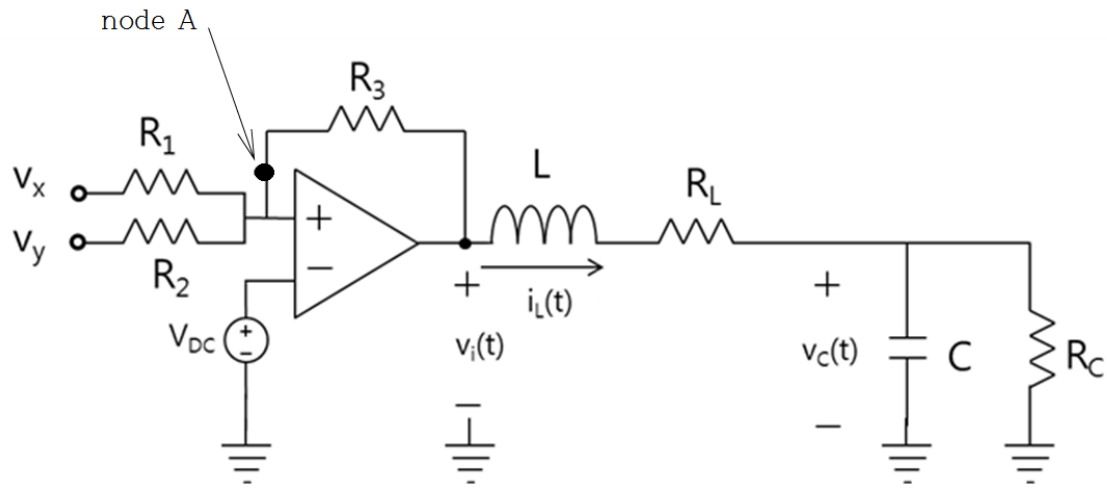(d)  $v_C(t)$

$$v_C = L \frac{di_L}{dt} + 2i_L$$

$$\begin{aligned} v_C &= \frac{d}{dt} \left( e^{-2t} \left( \frac{14}{5} \cos t + \frac{12}{5} \sin t \right) + \frac{1}{5} \cos 2t + \frac{8}{5} \sin 2t \right) + 2 \left( e^{-2t} \left( \frac{14}{5} \cos t + \frac{12}{5} \sin t \right) + \frac{1}{5} \cos 2t + \frac{8}{5} \sin 2t \right) \\ &= e^{-2t} \left( \frac{12}{5} \cos t - \frac{14}{5} \sin t \right) + \frac{14}{5} \sin 2t + \frac{18}{5} \cos 2t \end{aligned}$$



$v_x = 1.5u(t)$  [V],  $v_y = 3u(t)$  [V],  $V_{DC} = 3$  [V]

$R_1 = 2k\Omega$ ,  $R_2 = 4k\Omega$ ,  $R_3 = 8k\Omega$ ,  $R_L = 4 \Omega$ ,  $R_C = 2 \Omega$

$C = 0.125$  F,  $L = 4$  H

한글 해설지 (영문 해설지는 뒤에 있습니다/ English solution is provided on the last pages)

(a)  $V_i(t)$ 를 구하시오

op-amp의 특성에 따라 node A의 전위는  $V_{DC}$ 와 같다.

R1에 흐르는 전류 :  $I_{R_1} = \frac{V_x - V_{DC}}{R_1}$

R2에 흐르는 전류 :  $I_{R_2} = \frac{V_y - V_{DC}}{R_2}$

R3에 흐르는 전류 :  $I_{R_3} = \frac{V_x - V_{DC}}{R_1} + \frac{V_y - V_{DC}}{R_2}$

$$\begin{aligned}
 V_i(t) &= V_{DC} - R_3 I_{R_3} \\
 &= 3 - 4(1.5u(t) - 3) - 2(3u(t) - 3) \\
 &= 21 - 12u(t) [V]
 \end{aligned}$$

(2점)

(b)  $i_L(0^+)$ ,  $v_c(0^+)$ 를 구하시오

전류와 전압은 시간에 대해 연속이어야 하므로  $t=0^+$ 일 때  $\dot{i}_L$ 은  $t=0^-$ 일 때  $\dot{i}_L$ 과 같다  
 $t=0^-$ 일 때, L과 C가 평형상태에 도달하여 있으므로 L은 도선처럼 작용하고, C는 끊어진 회로로 작용한다.

$$i_L(0^+) = i_L(0^-) = \frac{21}{6} = \frac{7}{2} [A] \quad (2\text{점})$$

$$v_c(0^+) = v_c(0^-) = \frac{7}{2} \times 2 = 7 [V] \quad (2\text{점})$$



Δ시간:  $i_L, V_C$

$$9 - 4 \frac{di_L}{dt} - 4i_L - V_C = 0 \quad \text{--- ①}$$

$$i_L = \frac{1}{8} \frac{dV_C}{dt} + \frac{1}{2} V_C \quad \text{--- ②}$$

↙  
t3d18

$$\frac{di_L}{dt} = \frac{1}{8} \frac{d^2 V_C}{dt^2} + \frac{1}{2} \frac{dV_C}{dt} \rightarrow \text{①에 대입}$$

$$9 - 4 \left( \frac{1}{8} \frac{d^2 V_C}{dt^2} + \frac{1}{2} \frac{dV_C}{dt} \right) - 4 \left( \frac{1}{8} \frac{dV_C}{dt} + \frac{1}{2} V_C \right) - V_C = 0$$

$$9 - \frac{1}{2} \frac{d^2 V_C}{dt^2} - 2 \frac{dV_C}{dt} - \frac{1}{2} \frac{dV_C}{dt} - 2V_C - V_C = 0$$

$$-\frac{1}{2} \frac{d^2 V_C}{dt^2} - \frac{5}{2} \frac{dV_C}{dt} - 3V_C = -9$$

$$\frac{d^2 V_C}{dt^2} + 5 \frac{dV_C}{dt} + 6V_C = 18$$

$$\text{let } (V_C - 3) = P$$

$$\frac{d^2 V_C}{dt^2} = \frac{d^2 P}{dt^2}, \quad \frac{dV_C}{dt} = \frac{dP}{dt}$$

$$\frac{d^2 P}{dt^2} + 5 \frac{dP}{dt} + 6P = 0$$

$$\text{trial solution: } P(t) = e^{\lambda t}$$

$$\lambda^2 e^{\lambda t} + 5\lambda e^{\lambda t} + 6e^{\lambda t} = 0$$

$$\lambda^2 + 5\lambda + 6 = 0 \rightarrow \lambda = -2, -3$$

$$P(t) = A e^{-2t} + B e^{-3t}$$



$$V_c(t) = 3 + Ae^{-2t} + Be^{-3t}$$

초기조건 :  $V_c(0^+) = 7 \text{ V}$

$$7 = 3 + A + B \longrightarrow A + B = 4. \quad \text{--- (a)}$$

$$i_L(t) = \frac{1}{8} \frac{dV_c}{dt} + \frac{1}{2} V_c$$

$$= \frac{1}{8} (-2Ae^{-2t} - 3Be^{-3t}) + \frac{1}{2} (3 + Ae^{-2t} + Be^{-3t})$$

$$= \frac{3}{2} + \left(-\frac{A}{4} + \frac{A}{2}\right) e^{-2t} + \left(-\frac{3B}{8} + \frac{B}{2}\right) e^{-3t}$$

$$= \frac{3}{2} + \frac{A}{4} e^{-2t} + \frac{1}{8} B e^{-3t}$$

$$i_L(0^+) = \frac{7}{2} \text{ A}$$

$$\frac{7}{2} = \frac{3}{2} + \frac{A}{4} + \frac{1}{8} B \longrightarrow \frac{A}{4} + \frac{1}{8} B = 2$$

$$2A + B = 16 \quad \text{--- (b)}$$

①, ②를 풀면  $A = 12, B = -8$

$$\therefore V_c(t) = 3 + 12e^{-2t} - 8e^{-3t}$$

$$i_L(t) = \frac{3}{2} + 3e^{-2t} - e^{-3t}$$



Check

$$V_c(0^+) = 3 + 12 - 8 = 7 \quad \checkmark$$

$$V_c(\infty) = 3 \quad \checkmark$$

$$i_L(0^+) = \frac{3}{2} + 3 - 1 = \frac{7}{2} \quad \checkmark$$

$$i_L(\infty) = \frac{3}{2} \quad \checkmark$$

$$\mathcal{L} \rightarrow sF = f(s)$$



\*라플라스 변환을 쓰는 방법

$$9 - 4 \frac{di_L}{dt} - 4i_L - V_C = 0 \quad \dots (1)$$

$$i_L = \frac{1}{8} \frac{dV_C}{dt} + \frac{1}{2} V_C \quad \dots (2)$$

$$i_L(0^+) = \frac{7}{2}, \quad V_C(0^+) = 7$$

① 번식 라플라스변환 :  $\frac{9}{s} - 4(sI_L - \frac{7}{2}) - 4I_L - V_C = 0$

② 번식 라플라스변환 :  $I_L = \frac{1}{8}(sV_C - 7) + \frac{1}{2}V_C$

$$(4s+4)I_L + V_C = \frac{9}{s} + 14$$

$$-I_L + (\frac{s}{8} + \frac{1}{2})V_C = \frac{7}{8}$$

$$\begin{pmatrix} 4s+4 & 1 \\ -1 & \frac{s}{8} + \frac{1}{2} \end{pmatrix} \begin{pmatrix} I_L \\ V_C \end{pmatrix} = \begin{pmatrix} \frac{9}{s} + 14 \\ \frac{7}{8} \end{pmatrix}$$

$$\begin{pmatrix} I_L \\ V_C \end{pmatrix} = \frac{1}{(4s+4)(\frac{s}{8} + \frac{1}{2}) + 1} \begin{pmatrix} \frac{s}{8} + \frac{1}{2} & -1 \\ +1 & 4s+4 \end{pmatrix} \begin{pmatrix} \frac{9}{s} + 14 \\ \frac{7}{8} \end{pmatrix}$$



$$I_L = \frac{2}{s^2+5s+6} \times \frac{1s^2+9s+18}{4s} = \frac{\frac{1}{2}s^2 + \frac{29}{2}s + 9}{s(s+2)(s+3)}$$

$$V_C = \frac{2}{s^2+5s+6} \times \frac{1s^2+35s+18}{2s} = \frac{1s^2+35s+18}{s(s+2)(s+3)}$$

$$\begin{aligned} \text{i) } I_L &= \frac{\frac{1}{2}s^2 + \frac{29}{2}s + 9}{s(s+2)(s+3)} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+3} \\ &= \frac{(A+B+C)s^2 + (5A+3B+2C)s + 6A}{s(s+2)(s+3)} \end{aligned}$$

$$\left( \begin{array}{l} A+B+C = \frac{1}{2} \\ 5A+3B+2C = \frac{29}{2} \\ 6A = 9 \end{array} \right) \rightarrow \left( \begin{array}{l} A = 3/2 \\ B = 3 \\ C = -1 \end{array} \right)$$

$$I_L = \frac{3/2}{s} + \frac{3}{s+2} + \frac{-1}{s+3}$$

$$i_L(t) = \frac{3}{2} + 3e^{-2t} - e^{-3t} \quad (A)$$

$$\begin{aligned} \text{ii) } V_C &= \frac{1s^2+35s+18}{s(s+2)(s+3)} = \frac{D}{s} + \frac{E}{s+2} + \frac{F}{s+3} \\ &= \frac{(D+E+F)s^2 + (5D+3E+2F)s + 6D}{s(s+2)(s+3)} \end{aligned}$$

~~11/11/17~~

⇒



$$\begin{pmatrix} D+E+F=7 \\ 5D+7E+2F=35 \\ 6D=18 \end{pmatrix} \longrightarrow \begin{pmatrix} D=3 \\ E=12 \\ F=-8 \end{pmatrix}$$

$$N_e = \frac{3}{s} + \frac{12}{s+2} + \frac{-8}{s+3}$$

$$V_c(t) = 3 + 12e^{-2t} - 8e^{-3t} \text{ (V)}$$

(d)  $i_L(\infty)$ ,  $v_c(\infty)$ 를 구하시오

시간이 많이 흐르면 회로는 saturated되어 유도기는 도선처럼, 축전기는 끊어진 회로처럼 작용한다.

$$i_L(\infty) = \frac{9(V)}{6(\Omega)} = \frac{3}{2} [A] \text{ (2점)}$$

$$v_c(\infty) = \frac{3}{2} \times 2 = 3 [V] \text{ (2점)}$$



-----  
English Version

(a) find  $V_i(t)$

Due to characteristics of ideal op-amp, voltage of node A is same as  $V_{DC}$ .  
voltage of node A : 3V

$$\text{current through } R_1 : I_{R_1} = \frac{V_x - V_{DC}}{R_1}$$

$$\text{current through } R_2 : I_{R_2} = \frac{V_y - V_{DC}}{R_2}$$

$$\text{current through } R_3 : I_{R_3} = \frac{V_x - V_{DC}}{R_1} + \frac{V_y - V_{DC}}{R_2}$$

$$\begin{aligned} V_i(t) &= V_{DC} - R_3 I_{R_3} \\ &= 3 - 4(1.5u(t) - 3) - 2(3u(t) - 3) \\ &= 21 - 12u(t) \text{ [V]} \end{aligned}$$

(2points)

(b) find  $i_L(0^+)$  and  $v_c(0^+)$

Since current and voltage have to be continuous,  $i_L(0^+)$  is equal to  $i_L(0^-)$  and  $v_c(0^+)$  is equal to  $v_c(0^-)$ .

At  $t=0^-$ , the circuit is saturated and L can be substituted with a short line and C can substituted with a open circuit.

$$i_L(0^+) = i_L(0^-) = \frac{21}{6} = \frac{7}{2} \text{ [A]} \text{ (2points)}$$

$$v_c(0^+) = v_c(0^-) = \frac{7}{2} \times 2 = 7 \text{ [V]} \text{ (2points)}$$

(c) find  $i_L(t)$ ,  $v_C(t)$

Please check the Korean version

(d) find  $i_L(\infty)$ ,  $v_C(\infty)$

At  $t=\infty$ , the circuit is saturated. So L can be substituted with a short line and C can be substituted with an open circuit.

$$i_L(\infty) = \frac{9(V)}{6(\Omega)} = \frac{3}{2} [A] \text{ (2points)}$$

$$v_C(\infty) = \frac{3}{2} \times 2 = 3 [V] \text{ (2points)}$$




# Solution - Mid Term #2


[3]

(a) At steady-state, capacitance becomes open.  $\therefore V_m = -70.00 \text{ [mV]} \dots 2 \text{ pts}$

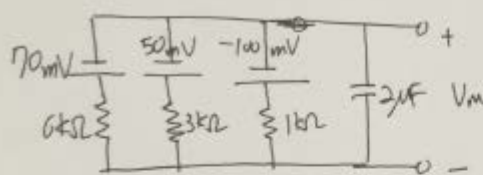(b)  $V_m(0^+) = V_m(0^-) = -70.00 \text{ [mV]} \dots 1 \text{ pt}$



Equivalent  
Circuit

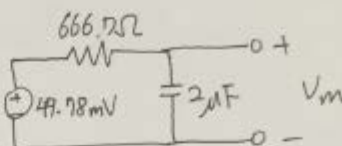

$$\therefore V_m(\infty) = 47.78 \text{ [mV]} \dots 1 \text{ pt}$$

$$\tau = RC = 1.334 \times 10^{-3} \text{ [sec]} \dots 1 \text{ pt}$$

$$\therefore V_m(t) = 47.78 - 117.8 e^{-\frac{t}{1.334 \cdot 10^{-3}}} \text{ [mV]} \dots 1 \text{ pt}$$

(c)  $V_m(3 \text{ msec}) = 35.35 \text{ mV} \dots 1 \text{ pt}$

$$V_m(\infty) = -96.29 \text{ mV}, R_t = 96.77 \Omega \rightarrow \tau = RC = 0.1935 \text{ ms} \dots 1 \text{ pt}$$


$$\therefore V_m(t) = -96.29 + 131.6 e^{-\frac{(t - 3.00 \cdot 10^{-3})}{0.1935 \cdot 10^{-3}}} \text{ [mV]} \dots 1 \text{ pt}$$

(d)  $V_m(5 \text{ msec}) = -96.29 \text{ mV} \dots 1 \text{ pt}$

$$V_m(\infty) = -70.00 \text{ mV} \dots 1 \text{ pt}$$

$$\tau = RC = 0.2000 \text{ ms} \dots 1 \text{ pt}$$
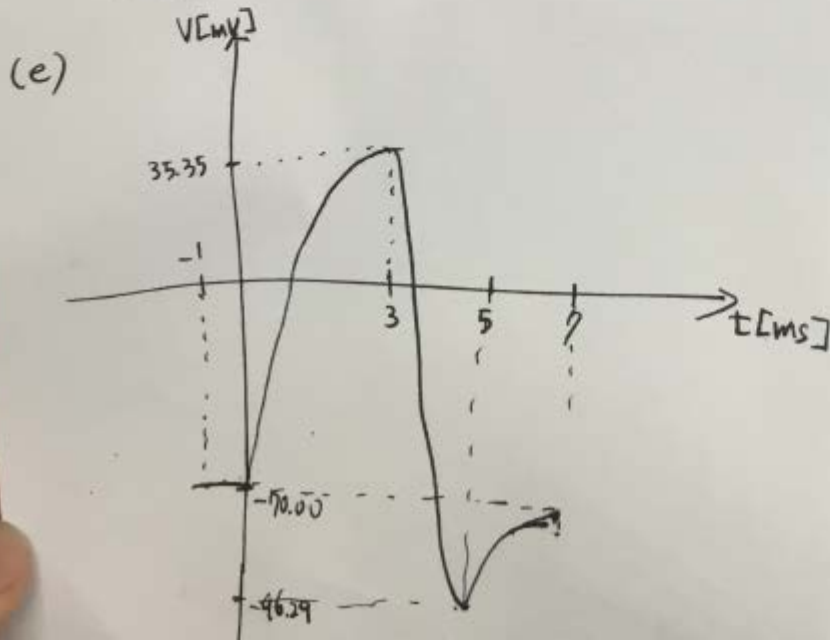
$$\therefore V_m(t) = -70.00 - 26.29 e^{-\frac{(t - 5 \cdot 10^{-3})}{0.2000 \cdot 10^{-3}}} \text{ [mV]} \dots 1 \text{ pt}$$




Graph 6점.

주요 point가 틀리거나  
안쓰면 -1점.


\* (a) ~ (e)

답에서 유효숫자 틀린 때마다  
-1점

[4] For the cascaded integrating amplifier below, answer the following questions.  
(Suppose the op-amp is ideal) (20pts)

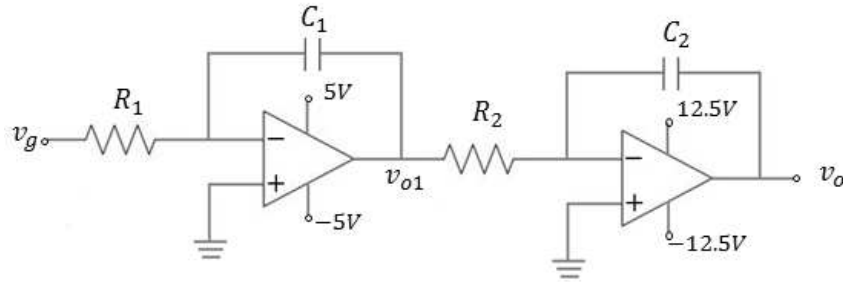

(figure 1) Cascaded integrating amplifier

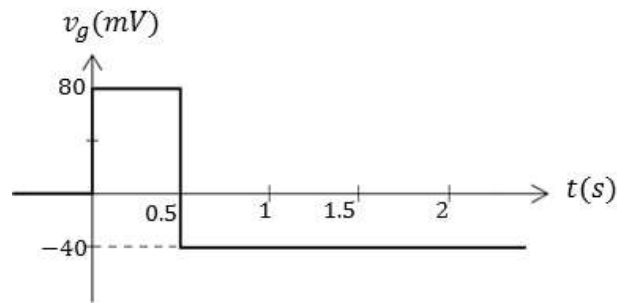

(figure 2)  $v_g - t$  graph

(a) Find the differential equations expressing the relations between  $v_g$  and  $v_{o1}$ ,  $v_g$  and  $v_o$ . (5pts)

By ideal op-amp & KCL,

$$\frac{v_g}{R_1} = -C_1 \frac{dv_{o1}}{dt} \quad \dots \textcircled{1} \text{ (+2pts)}$$

$$\frac{v_{o1}}{R_2} = -C_2 \frac{dv_o}{dt} \quad \dots \textcircled{2}$$

$$\textcircled{2} \text{를 } \textcircled{1} \text{에 대입하면 } v_g = -R_1 C_1 \frac{d}{dt} \left( -R_2 C_2 \frac{dv_o}{dt} \right)$$

$$\Rightarrow \frac{d^2 v_o}{dt^2} = \frac{1}{R_1 C_1} \frac{1}{R_2 C_2} v_g \text{ (+3pts, 사소한 실수 -1)}$$

(b) For the given  $v_g$  as in figure 2, find each  $v_{o1}(t)$ ,  $v_o(t)$  for  $0 \leq t \leq 0.5(s)$  and  $0.5 \leq t \leq t_{sat}$ . Suppose the  $R_1 C_1 = 50ms$ ,  $R_2 C_2 = 80ms$ , and initial charge of capacitor is zero. ( $t_{sat}$  is a saturation time when  $v_o$  is saturated to  $v_{ss}$  or  $-v_{ss}$ ) (10pts)

capacitor의 initial charge 0이므로,

$$v_{C_1}(0^-) = v_{C_1}(0^+) = 0, \quad v_{C_2}(0^-) = v_{C_2}(0^+) = 0 \text{이고, 따라서 } v_{o1}(0) = 0, \quad v_o(0) = 0$$

(초기조건 둘 다 맞은 경우 +1pt)

①  $0 \leq t \leq 0.5(s)$ 에서

$$\frac{dv_{o1}}{dt} = -\frac{v_g(t)}{R_1 C_1} = -1.6 \text{ 이므로 } v_{o1} = -1.6t [V] \quad (v_{o1}(0) = 0) \quad (+2pts)$$

$$\frac{d^2 v_o}{dt^2} = \frac{1}{R_1 C_1} \frac{1}{R_2 C_2} v_g(t) = 20 \text{ 이므로 } v_o(t) = 10t^2 [V] \quad \left( \frac{dv_o}{dt_{t=0}} = -\frac{1}{R_2 C_2} v_{o1}(0) = 0, \quad v_o(0) = 0 \right)$$

(+2pts)

$$t = 0.5s \text{에서 } v_{o1}(0.5) = -0.8V, \quad v_o(0.5) = 2.5V \quad (\text{경계조건 둘 다 맞은 경우 +1pt})$$

②  $0.5 \leq t \leq t_{sat}$ 에서

$$\frac{dv_{o1}}{dt} = -\frac{v_g(t)}{R_1 C_1} = 0.8 \text{ 이므로 } v_{o1} = 0.8t + A_1$$

$$v_{o1}(0.5) = 0.4 + A_1 = -0.8 \Rightarrow A_1 = -1.2$$

$$v_{o1}(t) = 0.8t - 1.2 [V] \quad (+2pts)$$

$$\frac{d^2 v_o}{dt^2} = \frac{1}{R_1 C_1} \frac{1}{R_2 C_2} v_g(t) = -10 \text{ 이므로 } v_o(t) = -5t^2 + A_2 t + A_3$$

$$\frac{dv_o(t)}{dt_{t=0.5}} = -\frac{1}{R_2 C_2} v_{o1}(0.5) = 10 = -5 + A_2 \Rightarrow A_2 = 15$$

$$v_o(0.5) = -1.25 + 0.5A_2 + A_3 = 2.5 \Rightarrow A_3 = -3.75$$

$$v_o(t) = -5t^2 + 15t - 3.75 [V] \quad (+2pts)$$

(c) Calculate the  $t_{sat}$ . (5pts)

$v_o(t) = -5(t - 1.5)^2 + 7.5$  이므로  $t_{sat}$  은  $v_o = -V_{ss} = -12.5$ 에 도달하는 시간 (+3pts, 이유 없으면 -2pt)

$$v_o(t_{sat}) = -5t_{sat}^2 + 15t_{sat} - 3.75 = -12.5$$

$$\Rightarrow t_{sat}^2 - 3t_{sat} - 1.75 = 0$$

$$\Rightarrow t_{sat} = 3.5s \quad (t > 0) \quad (+2pts)$$