

# Computer Organization

## **Single-cycle CPU**

Eunjin Baek, Pyeongsu Park

High Performance Computer System (HPCS) Lab

April 3<sup>rd</sup>, 2018


# Goals

- Understand the basic CPU structure.
- Understand the roles of **the datapath and the control unit**.
- Implement a single-cycle CPU in Verilog.


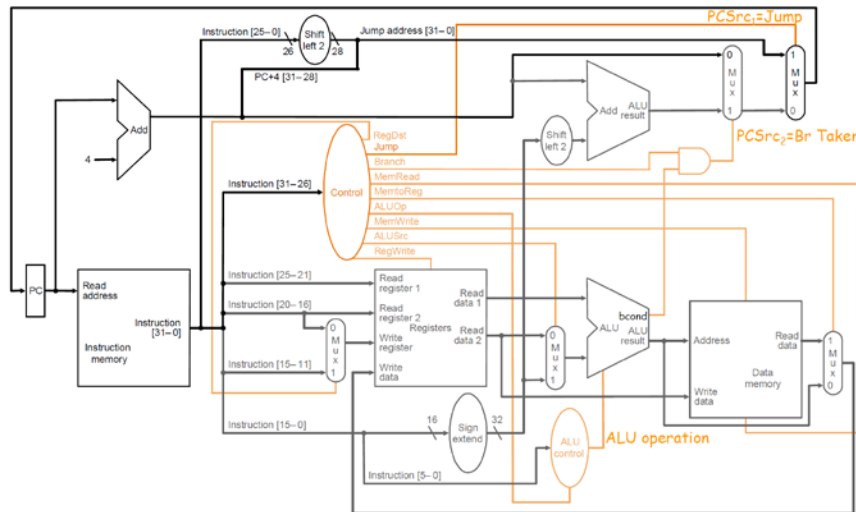
## Putting It All together

SNU EE430.322  
Spring '18 L5-28  
Jangwoo Kim




← Implement this slide!

# CPU structure: ISA

- Instruction Set Architecture (ISA)
  - Programmer visible state
  - User manual of the computer
- We will use **TSC ISA** instead of complicated MIPS ISA
  - 16-bit RISC ISA
  - Similar to MIPS, but more simplified
  - Refer to the manual on the eTL board
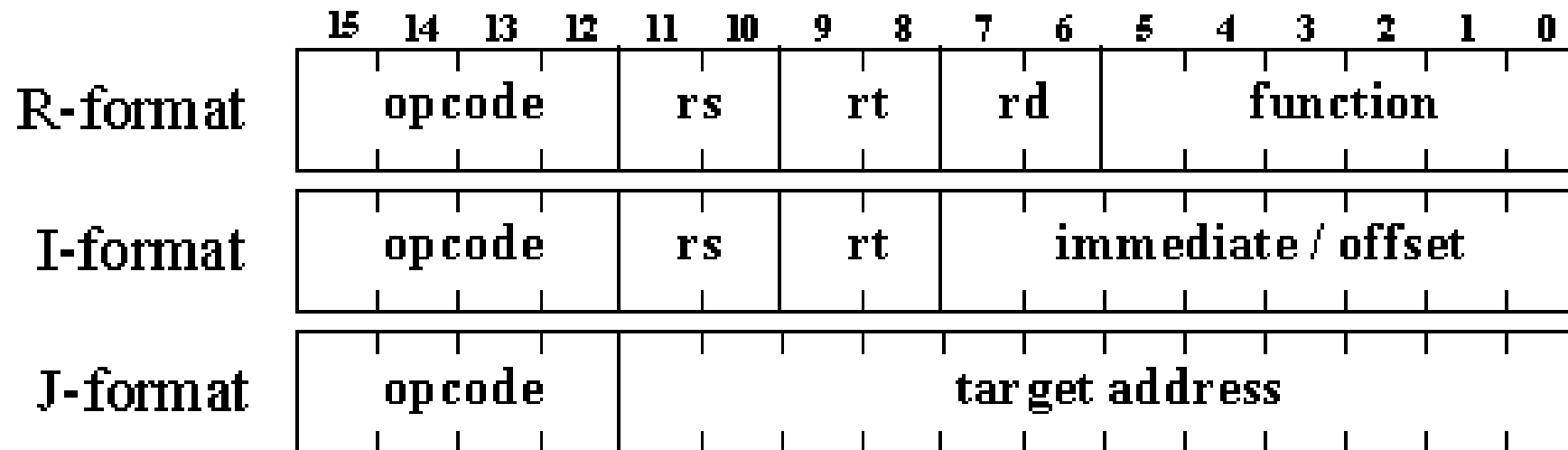
# TSC ISA

- Instruction types
  - R, I, and J-format
  - Similar to MIPS




# CPU structure: TSC ISA


- Instruction opcodes
  - Refer to the manual!

Instruction	Opcode	Function Code	Format
[ADD]	15	0	R
[SUB]	15	1	R
[AND]	15	2	R
[ORR]	15	3	R
[NOT]	15	4	R
[TCP]	15	5	R
[SHL]	15	6	R
[SHR]	15	7	R
[ADI]	4	-	I
[ORI]	5	-	I
[LHI]	6	-	I
[RWD]	15	27	R
[WWD]	15	28	R
[LWD]	7	-	I
[SWD]	8	-	I

# How to Make CPU?

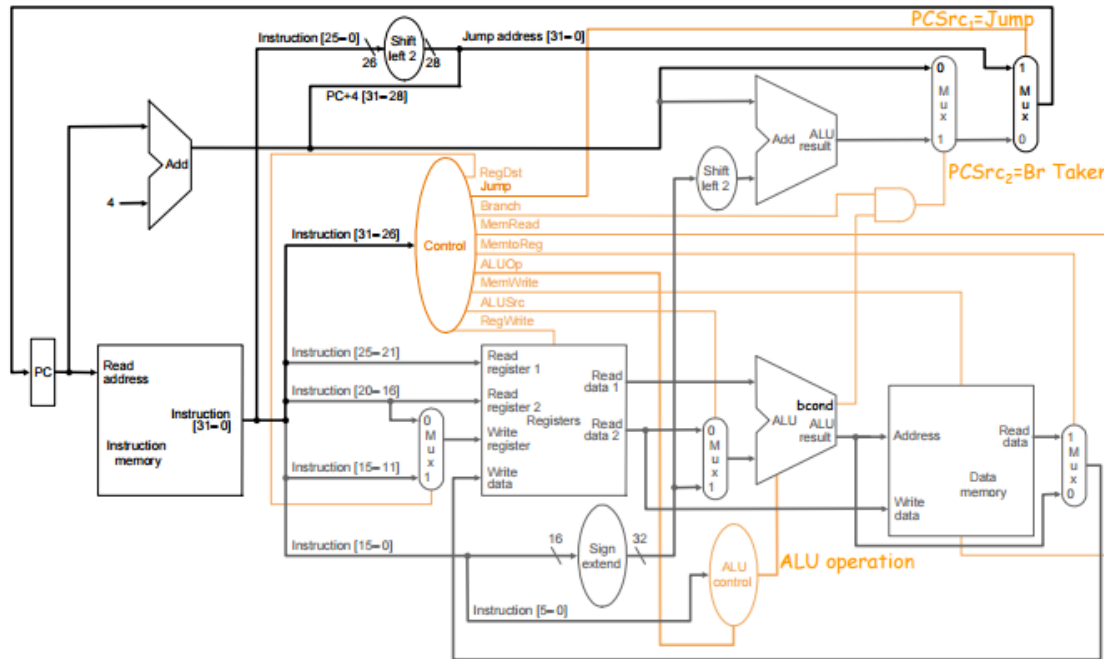

Simplified

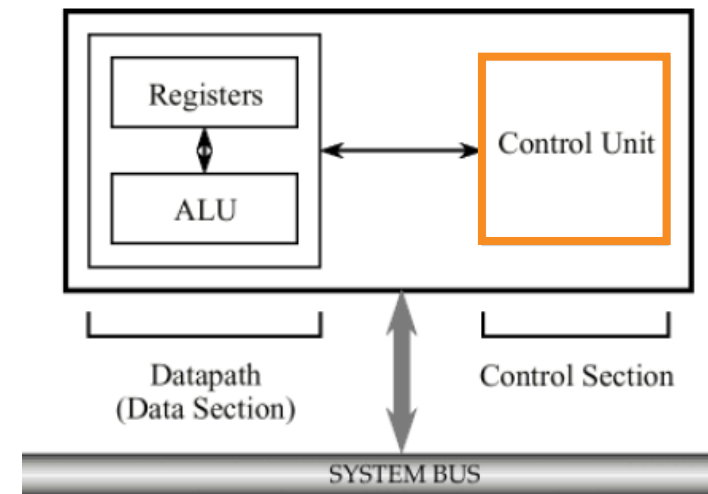


- Generally, CPU consists of two major components
  - **Datapath** (black boxes/lines) – Units in the path of data
  - **Control Unit** (orange boxes/lines) – Units which direct operations

# Datapath

- Datapath
  - Calculation: ALU
  - Data management: Register, Memory
- ❖ Register file (RF)
  - Read should be asynchronous to the clock. If you implement the RF synchronously, please change your design for the following projects.
- Chapter 4 of the textbook will be helpful to understand it 😊

# Control

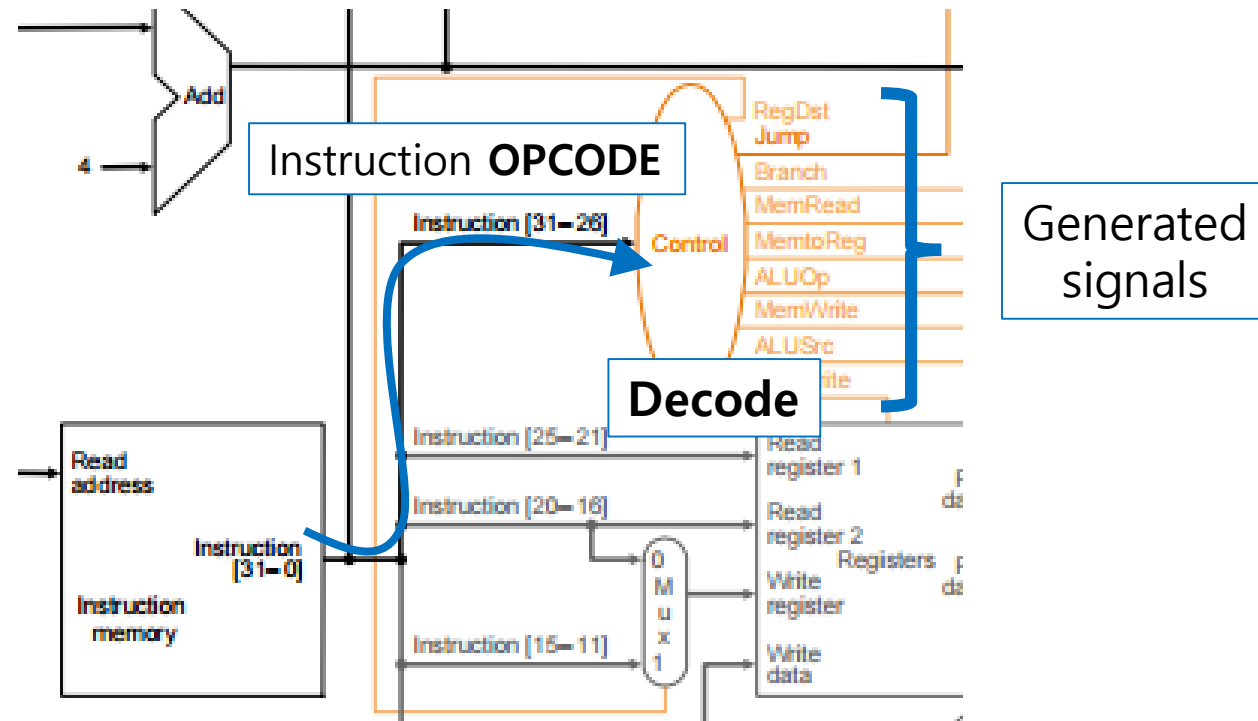

- Control unit
  - Decodes instruction
  - Generate the control signals for the datapath



# Assignment

- Implement a *single-cycle* TSC CPU.
  - A CPU that executes **one instruction per cycle**
  - **A datapath** for 16-bit CPU with four registers
  - **A control unit** to generate control signals used by the datapath
  - At this time, it has only five instructions (**ADD, ADI, LHI, JMP, WWD**)
- The datapath & the control unit should be clearly **separated**
  - Build them as two separate modules and connect them in the top module!
  - Control signals should transfer information between the datapath and the control unit.

# Tips: Implementation

```
// MODULE DECLARATION
module cpu (readM, address, data, inputReady, reset_n, clk, num_inst, output_port);
    output readM;      // read from memory
    output [`WORD_SIZE-1:0] address; // current address for data
    inout  [`WORD_SIZE-1:0] data;    // data being input or output
    input  inputReady; // indicates that data is ready from the input port
    input  reset_n;    // active-low RESET signal
    input  clk;        // clock signal

    // for debugging purpose
    output [`WORD_SIZE-1:0] num_inst; // number of instruction during execution
    output [`WORD_SIZE-1:0] output_port; // this will be used for a "WWD" instruction

    // ... fill in the rest of the code

endmodule
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
```

- We provide CPU skeleton code
  - Please refer to the comments for usages


# Tips: Implementation

---

```
// for debugging purpose  
output [`WORD_SIZE-1:0] num_inst;      // number of instruction during execution  
output [`WORD_SIZE-1:0] output_port; // this will be used for a "WWD" instruction
```

- output **num\_inst**
  - The number of instructions during an execution
  - For this project, you need to increment it for every posedge clock signals
- output **output\_port**
  - Used only for WWD instructions
  - WWD instructions [WWD \$rs] operates output port  $\leftarrow$  \$rs
- Testbench checks num\_inst and output\_port
  - Please refer to the given testbench file

# Tips: Implementation

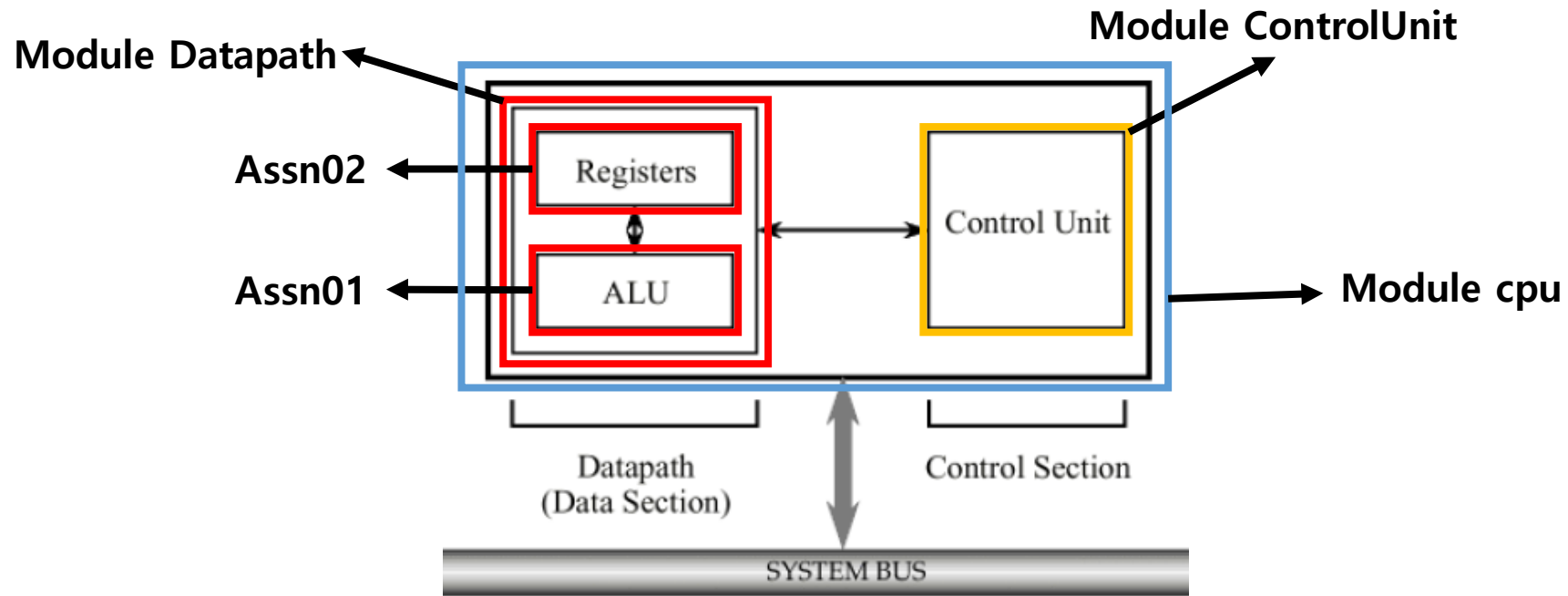

- Make your own "Datapath & ControlUnit" modules
  - The datapath module should contain an ALU module (Project 1) and a register file (Project 2)
  - The CPU module includes the datapath & the control unit modules

# Tips: Testbench


```
// model the read process for the memory device
assign data = readM ? outputData : `WORD_SIZE'bz;
always begin
    outputData = `WORD_SIZE'bz;
    #`PERIOD1;
    forever begin
        wait (readM == 1);
        #`READ_DELAY;
        outputData = memory[address];
        inputReady = 1;
        #(`STABLE_TIME);
        outputData = `WORD_SIZE'bz;
        inputReady = 0;
    end // of forever loop
end // of always block for memory read
```

- We also provide a testbench for the CPU module
  - It contains memory code and in-memory instructions for test-cases
 
# Testbench: Memory model


*data == outputData only when readM is 1.*

```
assign data = readM ? outputData : `WORD_SIZE'bz;
always begin
    outputData = `WORD_SIZE'bz;
    #`PERIOD;
    forever begin
        wait (readM == 1);
        #`READ_DELAY;
        outputData = memory[address];
        inputReady = 1;
        // $display("readM: %d, data: %d", outputData, data);
        #(`STABLE_TIME);
        outputData = `WORD_SIZE'bz;
        inputReady = 0;
    end // of forever loop
end // of always block for memory read
```


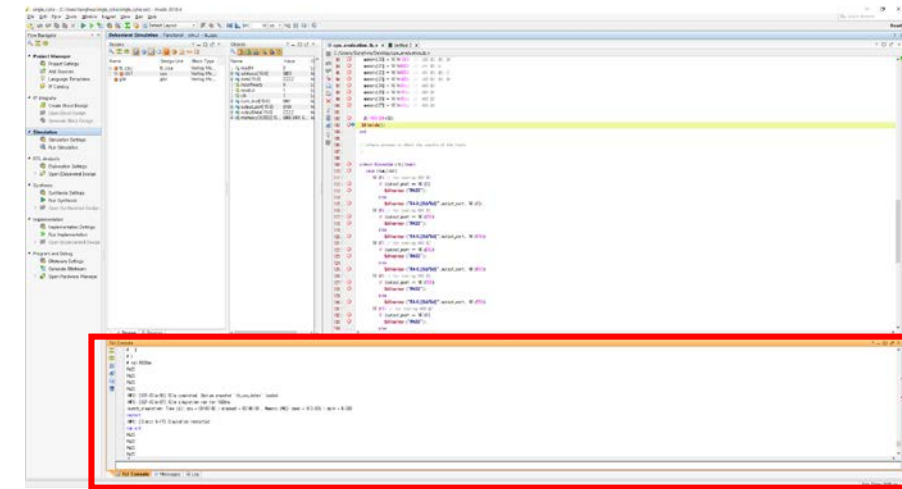
# Testbench (In-memory instructions)

```
// store programs and data in the memory
initial begin
    #`PERIOD1;    // delay for a while
    memory[0] = 16'h6000; // LHI $0, 0
    memory[1] = 16'h6101; // LHI $1, 1
    memory[2] = 16'h6202; // LHI $2, 2
    memory[3] = 16'h6303; // LHI $3, 3
    memory[4] = 16'hf01c; // WWD $0
    memory[5] = 16'hf41c; // WWD $1
    memory[6] = 16'hf81c; // WWD $2
    memory[7] = 16'hfc1c; // WWD $3
```



Tcl console

- We provide a testcase code on the eTL board
  - TSC instructions in memory
  - You can modify the code to write your program
  - You can check the result on Tcl console
    - If you pass the testcase, then "PASS" is printed on the console

**Thank You**