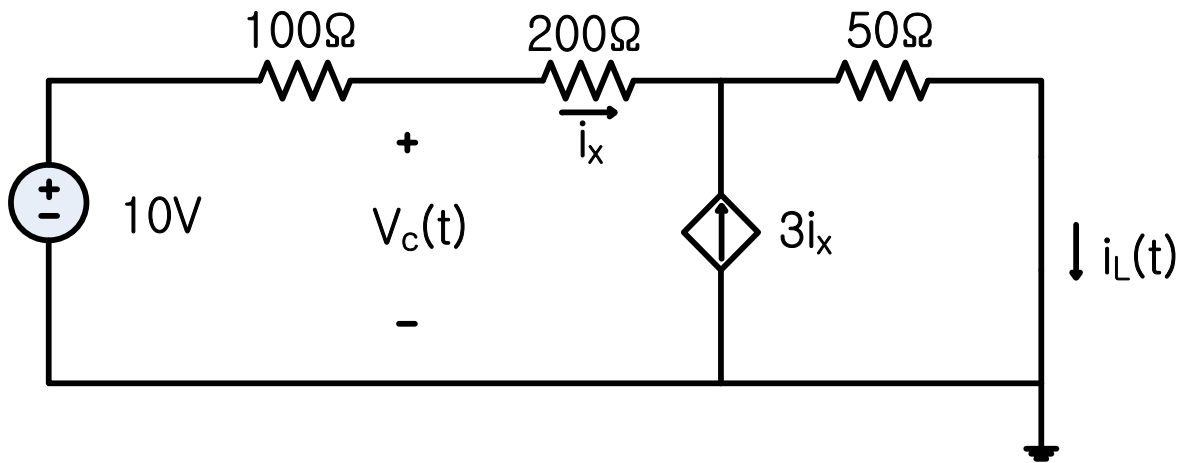


# # 1

(a)



KCL을 이용하면

$$10 = 100i_x(0^-) + 200i_x(0^-) + 50(i_x(0^-) + 3i_x(0^-))$$

$$\therefore i_x(0^-) = 0.02A$$

$$i_L(0^-) = i_x(0^-) + 3i_x(0^-) = 0.08A$$

$$V_c(0^-) = 10 - 100i_x(0^-) = 8V$$

(+2점)


inductor에서는 전류가 연속이고 capacitor에서 전압이 연속이어야 하므로

$$i_L(0^+) = i_L(0^-) = 0.08A$$

$$V_c(0^+) = V_c(0^-) = 8V$$

(각각 +1점)

(b)

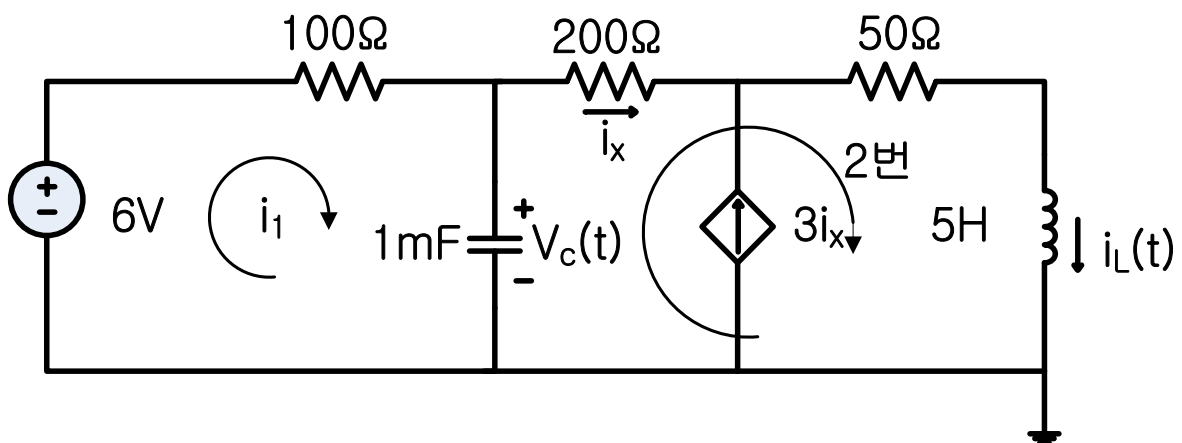

$$i_1 = i_x + 0.001 \frac{dV_c}{dt}$$

i<sub>1</sub>으로 KCL적용

$$6 = 100 \left( i_x + 0.001 \frac{dV_c}{dt} \right) + V_c$$

$$i_x = \frac{1}{4} i_L$$

$$6 = 25i_L + 0.1 \frac{dV_c}{dt} + V_c \quad (\text{식 1})$$

$$\therefore 6 = 100 \left( \frac{1}{4} i_L(0^+) + 0.001 \frac{dV_c(0^+)}{dt} \right) + V_c(0^+)$$

$$\frac{dV_c(0^+)}{dt} = -40V$$

(+2점)

Super mesh를 2번 loop로 적용

$$V_c = 200i_x + 50(i_x + 3i_x) + 5 \frac{di_L}{dt}$$

$$V_c = 100i_L + 5 \frac{di_L}{dt} \quad (\text{식 2})$$

$$\therefore \frac{di_L(0^+)}{dt} = 0A$$

(+2점)

(식 2)를 이용하여 V<sub>c</sub>를 (식 1) 통해 대입하면

$$6 = 25i_L + 0.1 \frac{d}{dt} (100i_L + 5 \frac{di_L}{dt}) + 100i_L + 5 \frac{di_L}{dt}$$

$$6 = 0.5 \frac{d^2 i_L}{dt^2} + 15 \frac{di_L}{dt} + 125i_L$$

$$\therefore \frac{d^2 i_L}{dt^2} + 30 \frac{di_L}{dt} + 250i_L = 12$$

(+4점)

(c)b에서 구한 식을 통해 먼저 Natural Response를 구한다.

$$\frac{d^2 i_L}{dt^2} + 30 \frac{di_L}{dt} + 250 i_L = 0$$

$$s^2 + 30s + 250 = 0$$

$$\therefore s = -15 \pm 5i$$

$$i_{L,n} = e^{-15t}(A \sin 5t + B \cos 5t)$$

(+1점)

Forced response는 dc이므로 assumed solution도 dc가 된다.

$$i_{L,f} = C$$

$$i_L(t) = e^{-15t}(A \sin 5t + B \cos 5t) + C$$

(+1점)

$$\frac{d^2 i_L}{dt^2} + 30 \frac{di_L}{dt} + 250 i_L = \frac{d^2 i_{L,n}}{dt^2} + 30 \frac{di_{L,n}}{dt} + 250 i_{L,n} + \frac{d^2 i_{L,f}}{dt^2} + 30 \frac{di_{L,f}}{dt} + 250 i_{L,f} = 0 + 250C = 12$$

$$C = 0.048$$

(+1점)

$$i_L(0^+) = 0.08 = B + C$$

$$B = 0.032$$

(+1점)

$$\frac{di_L(0^+)}{dt} = 0 = 5A - 0.48$$

$$A = 0.096$$

$$i_L(t) = e^{-15t}(0.096 \sin 5t + 0.032 \cos 5t) + 0.048$$


(+1점)

b에 (식 2)를 이용하여  $V_c(t)$ 를 구한다.

$$V_c(t) = 100 i_L(t) + 5 \frac{di_L(t)}{dt} = e^{-15t}(1.6 \sin 5t + 3.2 \cos 5t) + 4.8$$

(+3점)

#2

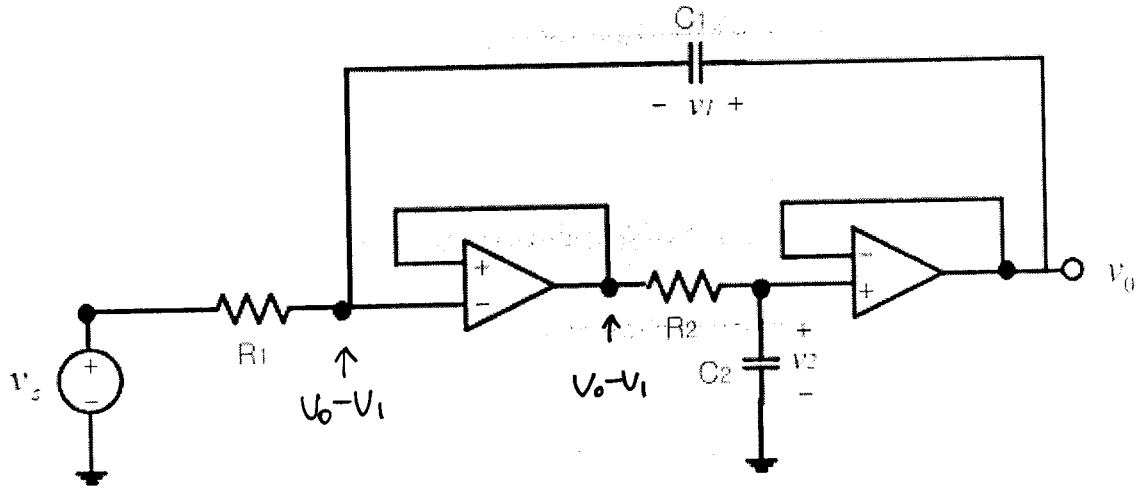

(a)  $v_o(t)$  회로방정식, damping coefficient, resonant frequency 구하기

$$\frac{V_0 - V_1 - V_s}{R_1} = C_1 \frac{dV_1}{dt} \quad \dots \textcircled{7} \rightarrow 1\text{점}$$

$$V_0 = V_2 \quad C_2 \frac{dV_0}{dt} + \frac{V_0 - (V_0 - V_1)}{R_2} = 0 \quad \dots \textcircled{8} \rightarrow 1\text{점}$$

$$\textcircled{7} \text{ 변경} \quad C_1 S V_1 = \frac{V_0 - V_1 - V_s}{R_1} \quad \dots \textcircled{9}$$

$$\textcircled{8} \text{ 변경} \quad C_2 S V_0 + \frac{V_1}{R_2} = 0 \quad \textcircled{2} \quad V_1 = -R_2 C_2 S V_0 \quad \dots \textcircled{10}$$

$\textcircled{10}$  을  $\textcircled{9}$  에 대입

$$R_1 C_1 S (-R_2 C_2 S V_0) = V_0 + R_2 C_2 S V_0 - V_s$$

$$R_1 R_2 C_1 C_2 S^2 V_0 + R_2 C_2 S V_0 + V_0 = V_s$$

$$S^2 V_0 + \frac{S V_0}{R_1 C_1} + \frac{V_0}{R_1 R_2 C_1 C_2} = \frac{V_s}{R_1 R_2 C_1 C_2}$$

$$\frac{d^2 V_0}{dt^2} + \frac{1}{R_1 C_1} \frac{dV_0}{dt} + \frac{1}{R_1 R_2 C_1 C_2} V_0 = \frac{1}{R_1 R_2 C_1 C_2} V_s \rightarrow 2\text{점}$$

$$2\alpha = \frac{1}{R_1 C_1} \quad \omega_0^2 = \frac{1}{R_1 R_2 C_1 C_2} \quad \alpha = \frac{1}{2R_1 C_1} \quad \omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

-(-)  $\rightarrow 2\frac{1}{2}$  점

(b)  $R_1 = 10 \text{ k}\Omega$   $R_2 = 20 \text{ k}\Omega$   $C_1 = 1 \text{ mF}$   $\frac{1}{2}$   $\frac{1}{2}$   $\frac{1}{2}$  overdamped  $\frac{1}{2}$   $\frac{1}{2}$

$$\alpha^2 > \omega_0^2$$

$$\alpha = \frac{1}{2R_1C_1}$$

$$\frac{1}{4R_1^2C_1^2} > \frac{1}{R_1R_2C_1C_2} \rightarrow 2\text{점}$$

$$C_2 > \frac{4R_1C_1}{R_2}$$

$$C_2 > 2 \text{ mF} \rightarrow 2\text{점}$$

(c)  $R_1 = 1 \text{ k}\Omega$   $C_1 = 2 \text{ mF}$   $R_2 = 1 \text{ k}\Omega$   $C_2 = 0.5 \text{ mF}$

$$\frac{d^2V_o}{dt^2} + \frac{1}{R_1C_1} \frac{dV_o}{dt} + \frac{1}{R_1R_2C_1C_2} V_o = \frac{1}{R_1R_2C_1C_2} V_S$$

$$\Rightarrow \frac{d^2V_o}{dt^2} + 500 \frac{dV_o}{dt} + 10^6 V_o = 10^6 V_S$$

$$s^2 + 500s + 10^6 = 0 \quad s = -250 \pm 250\sqrt{15}i$$

$$V_n = e^{-250t} (B_1 \cos 250\sqrt{15}t + B_2 \sin 250\sqrt{15}t) \quad \dots 2\text{점}$$

$$V_f = K \quad 10^6 K = 10^6 V_S \quad t \geq 0 \quad V_S = 10u(t) \\ K = 10 \quad \rightarrow V_S = 10$$

$$V_f = 10$$

$\dots 1\text{점}$

$$V_o(t) = V_n + V_f = e^{-250t} (B_1 \cos 250\sqrt{15}t + B_2 \sin 250\sqrt{15}t) + 10 \quad 2\text{점}$$

$$t=0 \text{ 일때 } V_2(0) = 0 = V_o(0)$$

$$t=0 \text{ 일때 } C_2 \frac{dV_o}{dt} + \frac{V_1}{R_2} = 0 \quad \frac{dV_o(0)}{dt} = 0$$


$$V_1(0) = 0$$

$$V_o(0) = 0 = B_1 + 10 = 0 \quad B_1 = -10$$

$$\frac{dV_o(0)}{dt} = 0 = -250B_1 + 250\sqrt{15}B_2 \quad B_2 = \frac{-10}{\sqrt{15}}$$

$$V_o(t) = e^{-250t} \left( -10 \cos 250\sqrt{15}t - \frac{10}{\sqrt{15}} \sin 250\sqrt{15}t \right) + 10 \quad \dots 3\text{점}$$
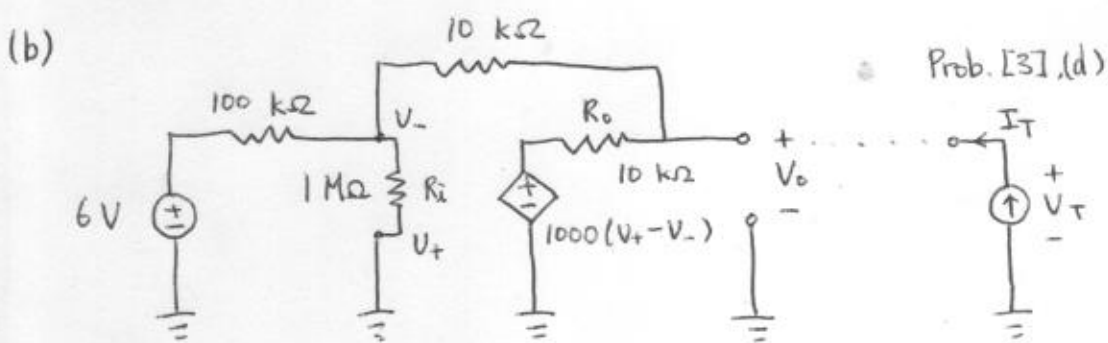
$$(a) \quad \dot{\lambda} = \frac{6-0}{100 \times 10^3}, \quad V_o = - \frac{6}{100 \times 10^3} \cdot 10^4 = -0.6 \text{ V}$$



(c) KCL at node ( $V_-$ ), node ( $V_o$ )

$$\frac{V_- - 6}{100 \times 10^3} + \frac{V_-}{10^6} + \frac{V_- - V_o}{10 \times 10^3} = 0$$

$$\frac{V_o - 1000(V_+ - V_-)}{10 \times 10^3} + \frac{V_o - V_-}{10 \times 10^3} = 0, \quad V_+ = 0$$


Eliminating  $V_-$ ,  $V_o = -\frac{9}{902} \cdot 60 = -0.5987 \text{ V}$

(d)

$$\frac{V_- - 6}{100 \times 10^3} + \frac{V_-}{10^6} + \frac{V_- - V_T}{10 \times 10^3} = 0$$

$$\frac{V_T - V_-}{10 \times 10^3} + \frac{V_T - (1000(V_+ - V_-))}{10 \times 10^2} - I_T = 0$$

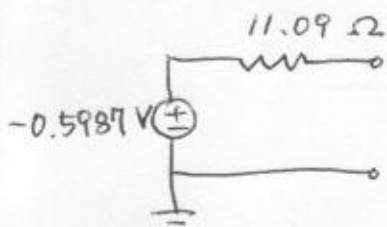
Eliminating  $V_-$ ,  $V_T = \frac{10^4}{902} \cdot I_T - \frac{540}{902}$




[4]

(a)  $\frac{6}{2 \times 10^{-3}} = -2 \times 10^{-6} \frac{dV_o(t)}{dt}, \quad V_o(0) = 0 \text{ V}$

$V_o(t) = -1500t \text{ V}$

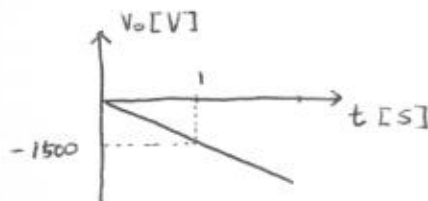


(b) sw = a,

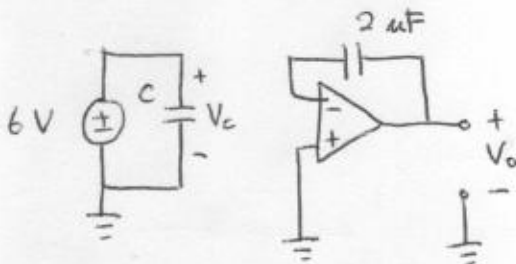

$V_c = 6 \text{ V}$

$C \frac{dV_o(t)}{dt} = 0 \quad \therefore V_o \text{ is constant}$

sw = b,

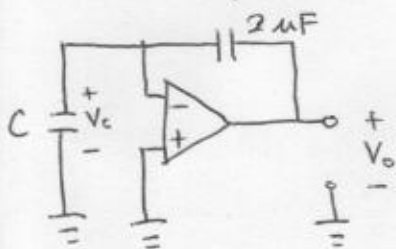


KCL:  $C \frac{dV_c}{dt} + 2 \times 10^{-6} \cdot \frac{d(-V_o)}{dt} = 0$

$\rightarrow \frac{dV_o}{dt} = \frac{C}{2 \times 10^{-6}} \cdot \frac{dV_c}{dt}$

Since, i) the accumulated charge in capacitor C is added to the capacitor of  $2 \mu\text{F}$ .

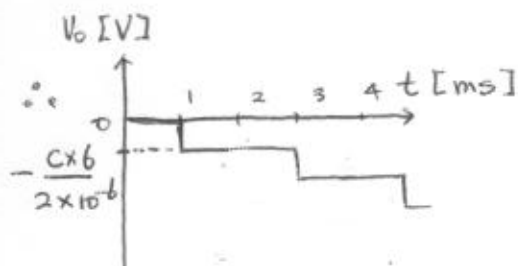ii)  $Q = CV, \quad \Delta V = \frac{\Delta Q}{C}$  when C is constant.


$\Delta V_o = \frac{C}{2 \times 10^{-6}} \cdot \Delta V_c = -\frac{C}{2 \times 10^{-6}} \cdot 6$



(c)  $-\frac{6 \cdot C}{2 \times 10^{-6}} = -1500, \quad C = 1 \mu\text{F}$

(d) Since the result of (a) and (c) are identical, switching capacitor can be viewed as 'resistor'

## Problem # 5

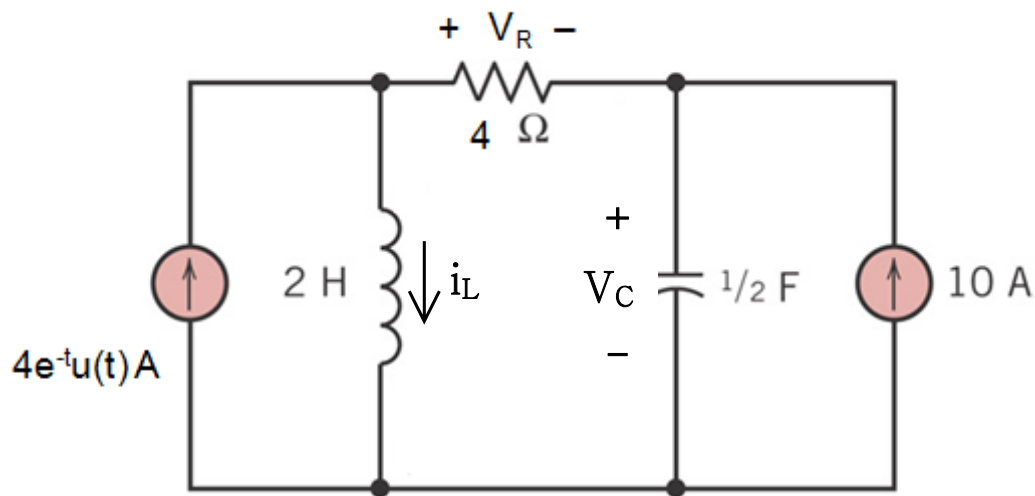

For  $t < 0$  (initial condition)

$$i_L(0^-) = 10 \text{ A} = i_L(0^+)$$

$$V_C(0^-) = 40 \text{ V} = V_C(0^+)$$

$t > 0$

$$V_C = V_L - V_R = 2 \frac{di_L}{dt} - V_R$$

$$i_L = 4e^{-t} - \frac{V_R}{4}$$

$$V_C = -8e^{-t} - \frac{2}{4} \frac{dV_R}{dt} - V_R$$

by KCL @ upper node of 10 A current source,

$$\begin{aligned} 10 &= i_C - \frac{V_R}{4} = \frac{1}{2} \frac{dV_C}{dt} - \frac{V_R}{4} \\ &= 4e^{-t} - \frac{1}{4} \frac{d^2 V_R}{dt^2} - \frac{1}{2} \frac{dV_R}{dt} - \frac{V_R}{4} \end{aligned}$$

$$\frac{d^2 V_R}{dt^2} + 2 \frac{dV_R}{dt} + V_R = 16e^{-t} - 40$$



*characteristic equation*

$$s^2 + 2s + 1 = 0$$

$$s = -1, -1$$

$$V_{R,n} = (A_1 + A_2 t) e^{-t}$$

$$V_{R,f} = K + B t^2 e^{-t}$$

$$\begin{aligned} 16e^{-t} - 40 &= K + B t^2 e^{-t} \\ &\quad + 2(2Bt - B t^2) e^{-t} \\ &\quad + (2B - 4Bt + B t^2) e^{-t} \\ &= K + 2B e^{-t} \end{aligned}$$

$$\therefore K = -40, B = 8$$

$$V_R(t) = (A_1 + A_2 t + 8t^2) e^{-t} - 40$$

$$\begin{aligned} V_C(0^+) &= -8 - \frac{2}{4} \frac{dV_R}{dt} \Big|_{0^+} - V_R(0^+) \\ &= -8 - \frac{1}{2} (-A_1 + A_2) - (A_1 - 40) \\ &= 32 - \frac{1}{2} A_1 - \frac{1}{2} A_2 = 40 \end{aligned}$$

$$\therefore A_1 + A_2 = -16$$

$$\begin{aligned} i_L(0^+) &= 4 - \frac{1}{4} V_R(0^+) \\ &= 4 - \frac{1}{4} (A_1 - 40) \\ &= 14 - \frac{1}{4} A_1 = 10 \end{aligned}$$

$$\therefore A_1 = 16, A_2 = -32$$

$$V_R(t) = (16 - 32t + 8t^2) e^{-t} - 40 \text{ [ V ]}$$

## Problem #6

(a)

Ideal OP-Amp has infinity gain ( $A_V = \infty$ )

Since OP-Amp has saturation voltage ( $\pm V_{sat}$ ),


$$V_o = \begin{cases} V_{sat} & (V_0 > V_{sat}) \\ V_o & (-V_{sat} < V_o < V_{sat}) \\ -V_{sat} & (V_0 < -V_{sat}) \end{cases}$$

$$V_o = A_V (V_+ - V_-) = A_V V_d$$

since  $A_V = \infty$ ,

$$V_o = \begin{cases} V_{sat} & (V_d > 0) \\ -V_{sat} & (V_d = 0) \\ -V_{sat} & (V_d < 0) \end{cases} \sim V_{sat}$$

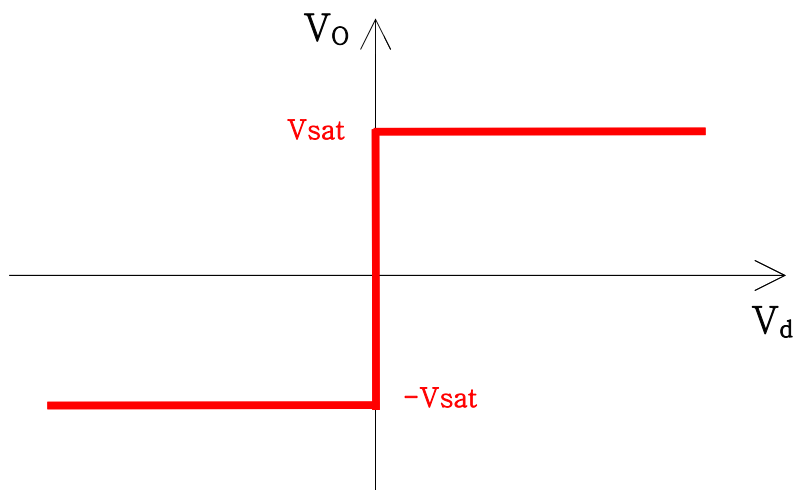Therefore, the relationship between  $V_d$  and  $V_o$  is




(b)

$$V_o = A_V (V_+ - V_-) = A_V (V_{in} - V_o)$$

$$V_o = \frac{A_V}{1 + A_V} V_{in} = V_{in} (\because A_V = \infty) \quad (-V_{sat} < V_o < V_{sat})$$

$$\therefore V_o = \begin{cases} V_{sat} & (V_{in} > V_o) \\ V_{in} & (V_{in} = V_o) \\ -V_{sat} & (V_{in} < V_o) \end{cases}$$

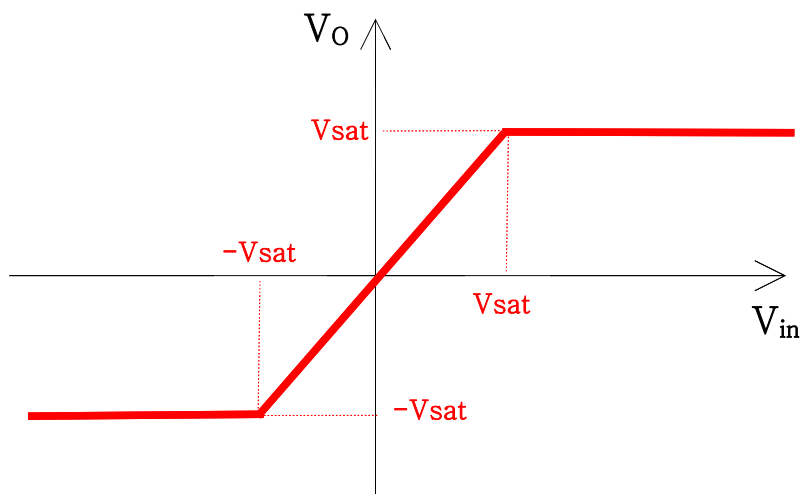Therefore, the relationship between  $V_{in}$  and  $V_o$  is




(c)

$$V_o = A_V (V_+ - V_-) = A_V (V_o - V_{in})$$

$$V_o = \frac{A_V}{-1 + A_V} V_{in} = V_{in} (\because A_V = \infty) \quad (-V_{sat} < V_o < V_{sat})$$

$$\therefore V_o = \begin{cases} -V_{sat} & (V_{in} > V_o) \\ V_{in} & (V_{in} = V_o) \\ V_{sat} & (V_{in} < V_o) \end{cases}$$

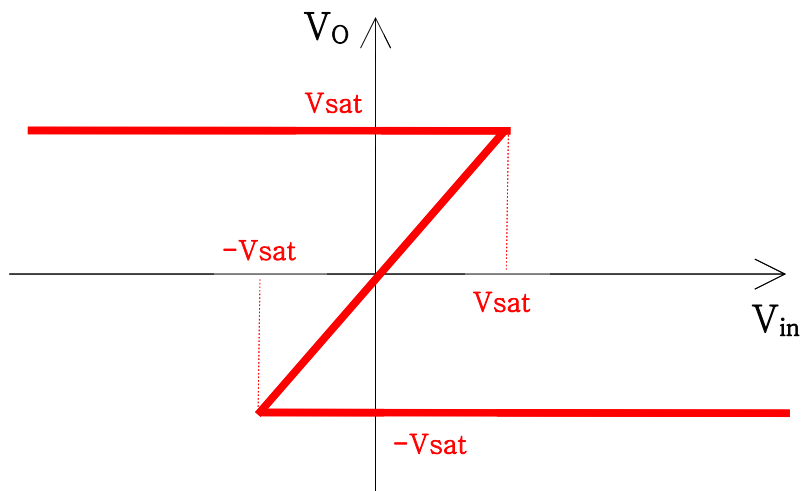Therefore, the relationship between  $V_{in}$  and  $V_o$  is



(d)

(b): negative feedback: feeding back part of the output (connected to  $V_-$ ) in such a way as to partially oppose the input  $\Rightarrow$  stable

(one input  $\rightarrow$  one output  $\Rightarrow$  stable)

(c): positive feedback: feeding back part of the output (connected to  $V_+$ ) so as to increase the input  $\Rightarrow$  unstable

(one input  $\rightarrow$  3 outputs for  $(-V_{sat} < V_{in} < V_{sat}) \Rightarrow$  unstable)