
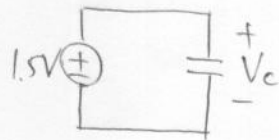


[1] (a)  $t < 0$ :

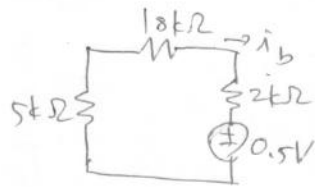


$$V_c(0^-) = 1.5 \text{ V} \dots \textcircled{1}$$



$$i_b(t) = \frac{-0.5 \text{ V}}{25 \text{ k}\Omega} = -\frac{2}{100} \text{ mA}$$

$t \geq 0$ :

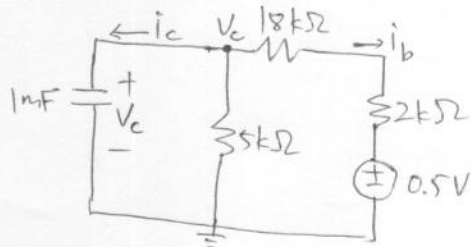

$$\text{KVL: } i_c + \frac{V_c}{5 \text{ k}\Omega} + \frac{V_c - 0.5}{20 \text{ k}\Omega} = 0.$$

$$i_c = \frac{1}{1000} \frac{dV_c}{dt}$$

$$\Rightarrow 4 \frac{dV_c}{dt} + V_c = \frac{1}{10}$$


$$\Rightarrow V_c = A e^{-\frac{t}{4}} + \frac{1}{10}$$

$$\text{by } \textcircled{1}, V_c(0) = A + \frac{1}{10} = 1.5. \Rightarrow A = 1.4$$

$$V_c(t) = 1.4 e^{-\frac{t}{4}} + 0.1$$

$$i_b(t) = \frac{V_c - 0.5}{20 \text{ k}\Omega} = \frac{7e^{-\frac{t}{4}} - 2}{100} \text{ (mA)}$$
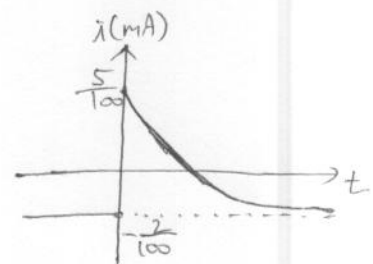
$$\therefore i_b(t) = \begin{cases} \frac{7e^{-\frac{t}{4}} - 2}{100} \text{ (mA)} & \text{at } t \geq 0 \\ -\frac{2}{100} \text{ (mA)} & \text{at } t < 0 \end{cases}$$



(b) Relay current  $= 50 i_b = \frac{7}{2} e^{-\frac{t}{4}} - 1 \text{ (mA)}$

The lamp turn off at 0.5 mA

$$\frac{7}{2} e^{-\frac{t}{4}} - 1 = 0.5$$

$$t \doteq 3.39 \text{ sec.}$$

[2] (a) KVL at node ①, ②:

$$\frac{V_1 - V_s}{\alpha R_1} + \frac{V_1 - V_2}{\alpha R_2} = 0$$


$$\frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_1}{R_L} = 0$$

$$\Rightarrow V_1 = -V_s \frac{R_L}{R_1}$$

$$V_2 = -V_s \frac{R_2 R_L}{R_1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_L} \right)$$

$$i_{out} = -\frac{V_1}{R_L}$$

$$i_{out} = V_s \cdot \frac{1}{R_1}$$

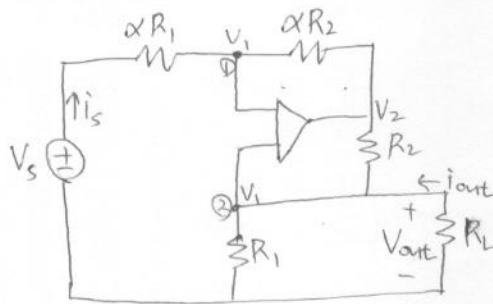

(b)

$$i_{out} = V_s \cdot \frac{1}{R_1}$$

$$\Rightarrow R_1 = 500 \Omega \quad (\text{from condition (ii)})$$

condition (i):  $i_s = \frac{V_s - V_1}{\alpha R_1} = V_s \cdot \frac{R_1 + R_L}{\alpha R_1^2} \leq 0.5 \text{ mA}$

$100 \Omega \leq R_L \leq 500 \Omega$ , so  $V_s \frac{R_1 + R_L}{\alpha R_1^2} \leq V_s \frac{R_1 + 500}{\alpha R_1^2}$

$\therefore V_s \frac{R_1 + 500}{\alpha R_1^2} \leq 0.5$  to satisfy condition (i)

$$5 \cdot \frac{500 + 500}{\alpha \cdot 500^2} \leq 0.5$$

$$\alpha \geq 40$$

condition (iii):  $|V_2| = V_s \cdot \frac{R_2 R_L}{R_1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_L} \right) \leq 20$

$|V_2|$  is maximum at  $R_L = 500 \Omega$ .

$$\therefore 5 \cdot \frac{R_2 \cdot 500}{500} \left( \frac{1}{500} + \frac{1}{R_2} + \frac{1}{500} \right) \leq 20$$

$$R_2 \leq 750 \Omega$$

$\therefore R_1 = 500 \Omega$

$R_2 \leq 750 \Omega$

$\alpha \geq 40$

1. (a) 랑자 a와 b 사이의 Thevenin 등가 회로를 구하십시오.




$$-5R_x - 10V_o - R_x V_{th} = 0$$

$$3V_{th} - 2V_o = 0 \quad V_o = \frac{3}{2} V_{th}$$

$$V_{th} = \frac{-5Rx}{Rx + 15}$$

(1)  $I_{SC}$  구하기

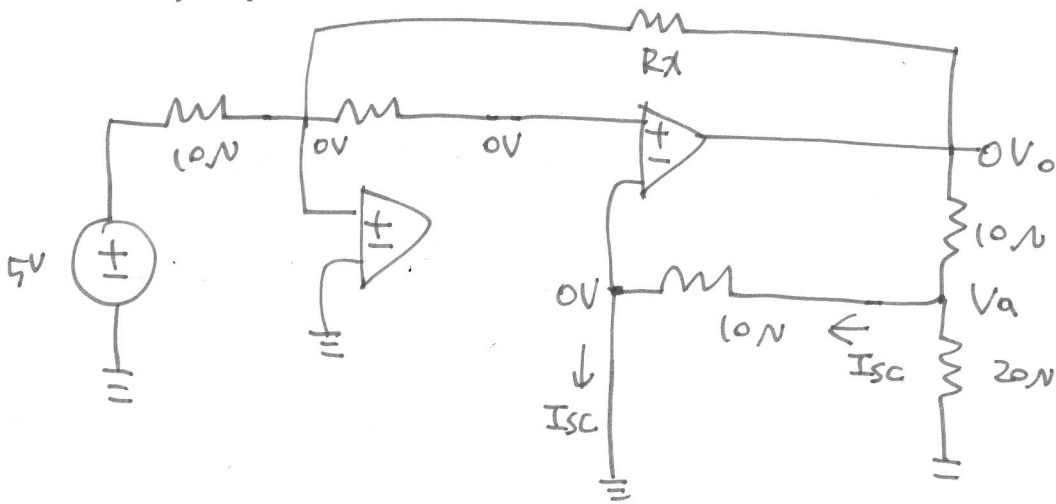

$$\frac{0-5}{10} + \frac{0-V_o}{R_x} = 0$$

$$V_o = -\frac{1}{2} R_x$$


$$\frac{V_a}{10} + \frac{V_a}{20} + \frac{V_a - V_o}{10} = 0$$

$$2V_a + V_a + 2V_a - 2V_o = 0$$


$$5V_a = 2V_o$$

$$I_{SC} = \frac{V_a}{10} = \frac{2V_o/5}{10} = \frac{1}{25} V_o = -\frac{1}{50} R_x$$
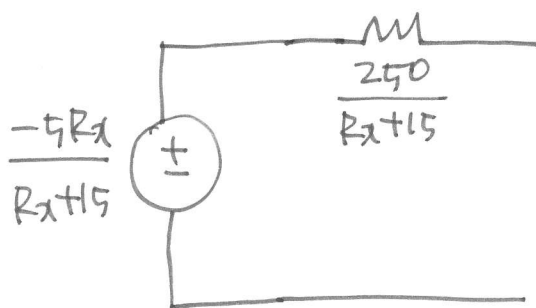
$$R_{th} = \frac{V_{th}}{I_{SC}} = \frac{\frac{-5R_x}{R_x+15}}{-\frac{1}{50} R_x} = \frac{250}{R_x+15}$$




(b)

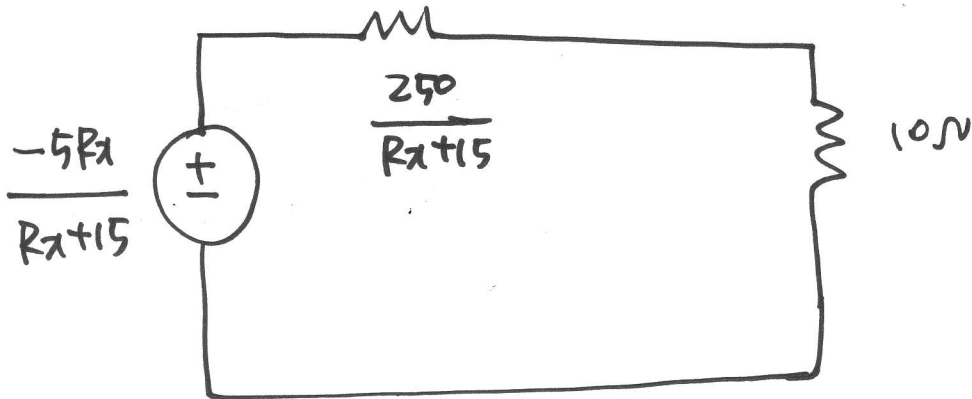

$$P = \left( \frac{\frac{-5R_x}{R_x + 15}}{\frac{250}{R_x + 15} + 10} \right)^2 \cdot 10$$

$$= \left( \frac{-R_x}{2R_x + 80} \right)^2 \cdot 10$$

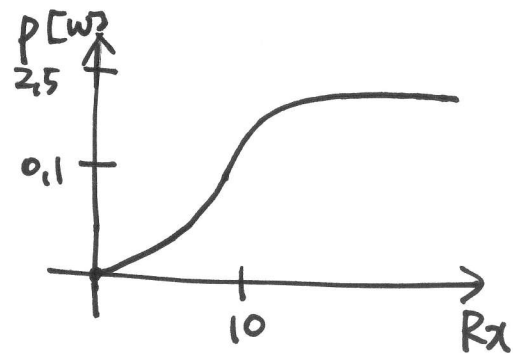
$$\frac{dP}{dR_x} = \frac{1600 R_x}{(2R_x + 80)^3}$$



$$R_x \rightarrow \infty \quad P = 2.5 \text{ W}$$

3점                      1점

1점 / 4점

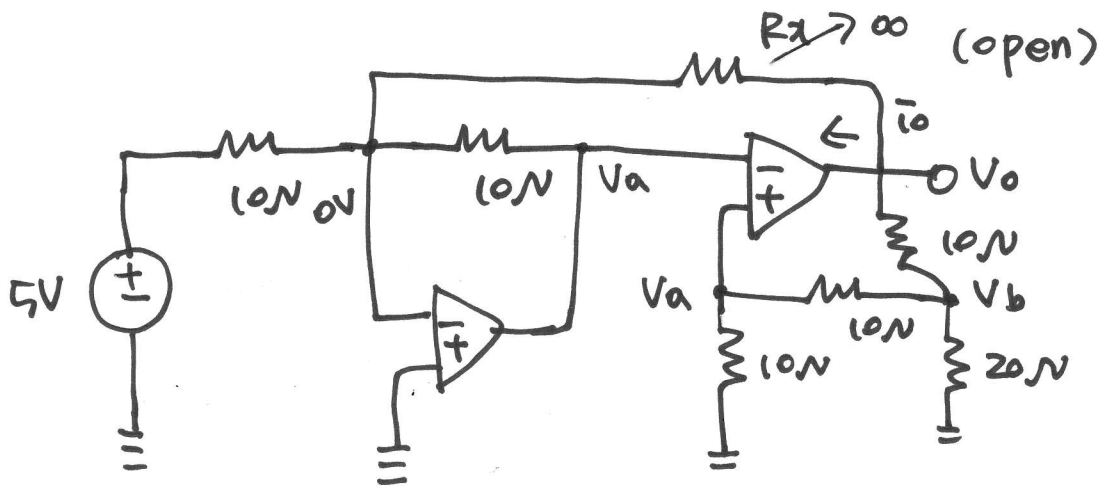

$$\frac{0-5}{10} + \frac{0-V_a}{10} = 0 \quad V_a = -5V$$

$$\frac{V_a}{10} + \frac{V_a - V_b}{10} = 0 \quad V_b = 2V_a = -10V$$

$$\bar{i}_0 + \frac{V_0 - V_b}{10} = 0$$

$$\frac{V_b - V_a}{10} + \frac{V_b}{20} + \frac{V_b - V_0}{10} = 0$$

$$2V_b - 2V_a + V_b + 2V_b - 2V_0 = 0$$

$$5V_b - 2V_a = 2V_0 \quad V_0 = -20V \rightarrow 3\text{점}$$

$$\bar{i}_0 = \frac{V_b - V_0}{10} = \frac{10}{10} = 1A \rightarrow 3\text{점}$$


2점

$\bar{i}_0, V_0$  각각 2점

$\bar{i}_0, V_0$  각각 1점

[4]

(1) 회로망의 방정식

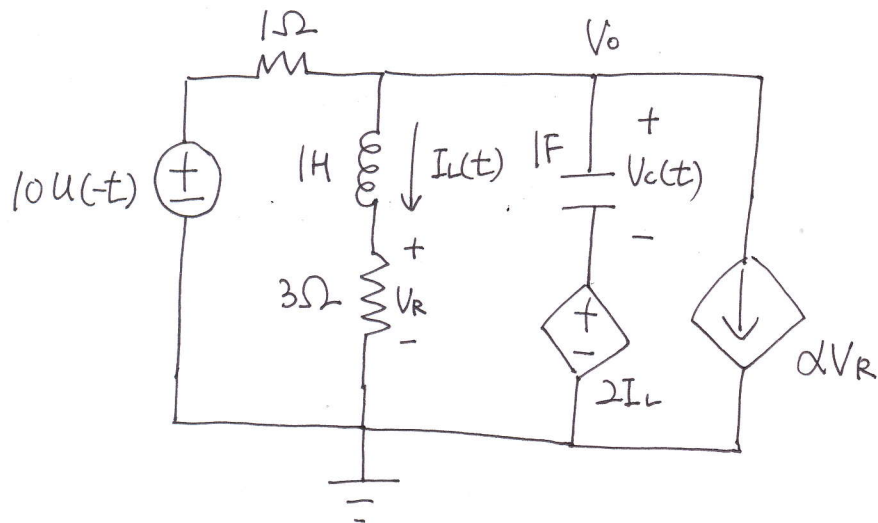

$$\textcircled{1} \quad \frac{dI_L}{dt} + 3I_L = V_C + 2I_L = V_0$$

$$V_C = \frac{dI_L}{dt} + I_L \quad \text{---} \textcircled{2}$$

$V_0$ 에 KCL

$$\textcircled{2} \quad \frac{V_0}{1} + I_L + 3\alpha \cdot I_L + \frac{dV_C}{dt} = 0$$

①의 식 대입

$$(3I_L + \frac{dI_L}{dt}) + I_L + 3\alpha I_L + \frac{dV_C}{dt} = 0$$

$$(4 + 3\alpha)I_L + \frac{dI_L}{dt} + \frac{dV_C}{dt} = 0$$

$$\text{특성방정식} : s^2 + 2s + (4 + 3\alpha) = 0$$

1)

(2)

① Overdamped

$$\alpha < -1 \text{ and } -1 + \sqrt{-3(\alpha+1)} < 0$$

$$-\frac{4}{3} < \alpha < -1$$

② Critically damped

$$-3(\alpha+1) = 0 \quad \alpha = -1$$

③ Underdamped

$$-3(\alpha+1) < 0$$

$$\alpha + 1 > 0$$


$$\alpha > -1$$

2)



(3)  $\alpha = 2$  일때 초기 조건

$V_C(0^-)$ ,  $I_L(0^-)$  계산

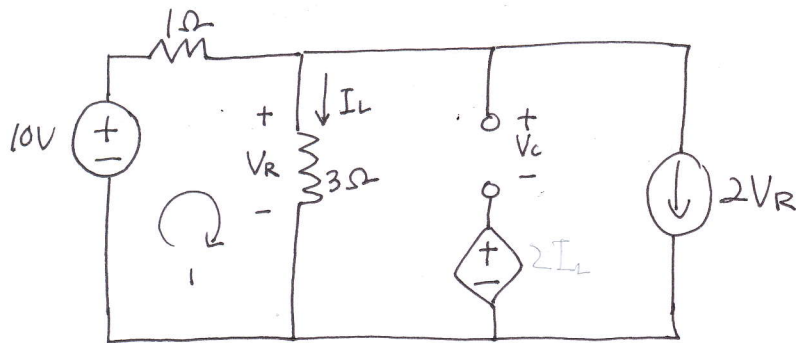

여기서 KVL

$$10 = 1(I_L + 2V_R) + 3I_L \quad V_R = 3I_L \quad I_L(0^-) = 1A$$

$$= 10I_L \quad V_C(0^-) = 1V$$

$$V_C + 2I_L = 3$$

$$I_L(t) = A_1 e^{-t} \cos 3t + A_2 e^{-t} \sin 3t = e^{-t} (A_1 \cos 3t + A_2 \sin 3t)$$

$$I_L(0^-) = 1 \Rightarrow A_1 = 1$$

$$I_L'(t) = -e^{-t} (A_1 \cos 3t + A_2 \sin 3t) + e^{-t} (-3A_1 \sin 3t + 3A_2 \cos 3t)$$

$$I_L'(0) = -A_1 + 3A_2 = 0 \quad A_2 = \frac{1}{3}$$

앞의 식에서 (회로 방정식)  $V_C(t) = \frac{dI_L(t)}{dt} + I_L(t)$

$$I_L'(0) = 0$$


$$I_L(t) = e^{-t} \cos 3t + \frac{1}{3} e^{-t} \sin 3t$$

$$V_C(t) = \frac{dI_L}{dt} + I_L$$

$$= -\frac{10}{3} e^{-t} \sin 3t + e^{-t} \cos 3t + \frac{1}{3} e^{-t} \sin 3t$$

$$= -3e^{-t} \sin 3t + e^{-t} \cos 3t$$

[5] Method I; Direct Method.

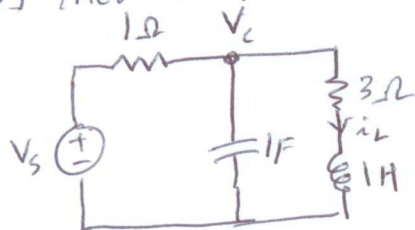

KCL at node  $V_c$ .

$$\frac{V_s - V_c}{1} = \frac{dV_c}{dt} + i_L, \quad V_c = 3i_L + \frac{di_L}{dt}$$

$$\Rightarrow V_s = 4i_L + 4\frac{di_L}{dt} + \frac{d^2 i_L}{dt^2}$$

Homogeneous solution,  $i_{L,H}(t) = Ae^{-2t} + Be^{-2t}$

Particular solution,  $i_{L,p}(t) = Ct^2 e^{-2t}$

Total solution,  $i_L(t) = i_{L,H}(t) + i_{L,p}(t) = (A + Bt + Ct^2)e^{-2t}$

If  $t < 0$ ;  $i_L(0^-) = 1A$  ( $\because V_s(0^-) = 4V$ ,  $i_L(0^-) = \frac{4V}{4\Omega} = 1A$ )

$i_L(0^-) = i_L(0^+) \rightarrow$  continuity for inductor

$$V_c(0^-) = V_c(0^+) \Leftrightarrow 3i_L(0^-) + \left. \frac{di_L}{dt} \right|_{t=0^-} = 3i_L(0^+) + \left. \frac{di_L}{dt} \right|_{t=0^+}$$

$$\therefore \left. \frac{di_L}{dt} \right|_{t=0^-} = \left. \frac{di_L}{dt} \right|_{t=0^+} = 0 \quad (\because t < 0, \frac{di_L}{dt} = 0)$$

$\therefore$  Boundary Condition for  $i_L(t)$

①  $i_L(0) = 1A$

②  $i_L'(0) = 0$

$\Rightarrow$  we can find A and B in equation of  $i_L(t)$

$$A = 1, \quad -2A + B = 0 \quad \therefore B = 2$$

In addition, we can also find C by Particular solution,


$$\frac{d^2}{dt^2} (Ct^2 e^{-2t}) + 4 \frac{d}{dt} (Ct^2 e^{-2t}) + 4(Ct^2 e^{-2t}) = e^{-2t} = V_s(t)$$

$$\Leftrightarrow (2Ce^{-2t} - 8Cte^{-2t} + 4Ct^2 e^{-2t}) + 4(2Cte^{-2t} - 2Ct^2 e^{-2t}) + 4(Ct^2 e^{-2t}) = e^{-2t}$$

$$\Leftrightarrow 2Ce^{-2t} = e^{-2t} \quad \therefore C = 0.5$$

$$\therefore i_L(t) = e^{-2t} + 2te^{-2t} + 0.5t^2 e^{-2t} \quad (A)$$

[5] Method II; Impedance.

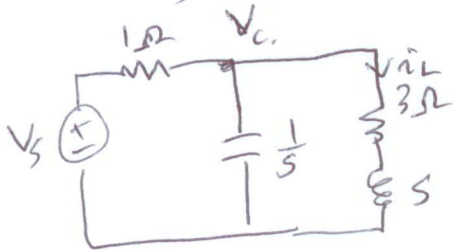

$$\hat{I}_L = \frac{V_s}{\text{total impedance}} \times \frac{\frac{1}{s}}{3+s+\frac{1}{s}}$$

$$\text{total impedance} = \frac{1}{s} \parallel (3+s) + 1$$

$$= \frac{\frac{1}{s}(3+s)}{\frac{1}{s} + 3 + s} + 1 = \frac{s+3}{s^2+3s+1} + 1$$


$$= \frac{s^2+4s+4}{s^2+3s+1}$$

$$\therefore \hat{I}_L = V_s \cdot \frac{\cancel{s^2+3s+1}}{s^2+4s+4} \times \frac{1}{\cancel{s^2+3s+1}}$$

$$\therefore V_s = \hat{I}_L (s^2+4s+4)$$

$\Rightarrow$  Same as method I.

[5] 1μF 0.2Ω 회로,

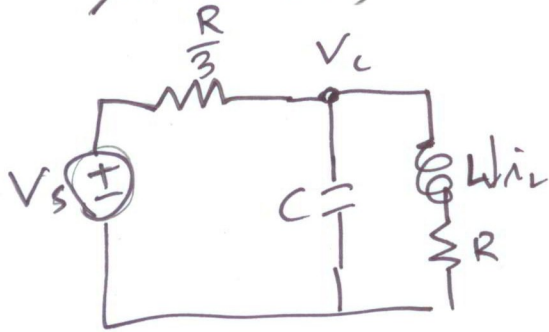

$$\frac{V_s - V_c}{\frac{R}{3}} = C \frac{dV_c}{dt} + \dot{i}_L$$

$$V_c = L \frac{d\dot{i}_L}{dt} + R\dot{i}_L$$

$$\Rightarrow V_s = \frac{RC}{3} L \frac{d^2 \dot{i}_L}{dt^2} + \left(L + \frac{R^2 C}{3}\right) \frac{d\dot{i}_L}{dt} + \frac{4}{3} R \dot{i}_L$$

$$\Rightarrow e^{-2t} = \mu \frac{d^2 \dot{i}_L}{dt^2} + (1+3\mu) \frac{d\dot{i}_L}{dt} + 4\dot{i}_L$$

일반해,  $\dot{i}_{L,H} = A e^{\alpha t} + B e^{\beta t}$

특수해  $\dot{i}_{L,P} = C e^{-2t}$

$$\therefore \dot{i}_L(t) = A e^{\alpha t} + B e^{\beta t} + C e^{-2t}$$

$$\alpha = \frac{-(1+3\mu) + \sqrt{(1+3\mu)^2 - 16\mu}}{2\mu} \approx -4$$

$$\beta = \frac{-(1+3\mu) - \sqrt{(1+3\mu)^2 - 16\mu}}{2\mu} \approx -1000000$$

★ 상수 A, B, C 구하기.

Boundary condition;  $\dot{i}_L(0) = 1A$ ,  $\left. \frac{d\dot{i}_L}{dt} \right|_{t=0} = 0$

• 상수 C 구하기;  $\dot{i}_L(t) = C e^{-2t}$  대입;

$$(4\mu + (-2-6\mu) + 4)C = 1 \quad \therefore \begin{cases} C = \frac{1}{2-2\mu} \\ C \approx 0.5 \quad (24) \end{cases}$$

• 상수 A, B 구하기; Boundary condition 이용.

(i)  $\dot{i}_L(0) = 1 \Rightarrow A + B + C = 1 \Rightarrow A + B = -(-1) = 1 - \frac{1}{2-2\mu} \dots (1)$


(ii)  $\dot{i}_L'(0) = 0 \Rightarrow \alpha A + \beta B - 2C = 0 \Rightarrow \alpha A + \beta B = 2C = \frac{1}{1-\mu} \dots (2)$

①, ② 연립하면,  $A = \frac{\beta(1-2\mu)}{\alpha-\beta}$ ,  $B = \frac{-\alpha(1-2\mu)}{\alpha-\beta}$   
 $A \approx 0.5$ ,  $B \approx -3\mu$

$$\therefore \dot{i}_L(t) \approx 0.5 e^{-4t} - 3\mu e^{-1000000t} + 0.5 e^{-2t} [A]$$



[6]

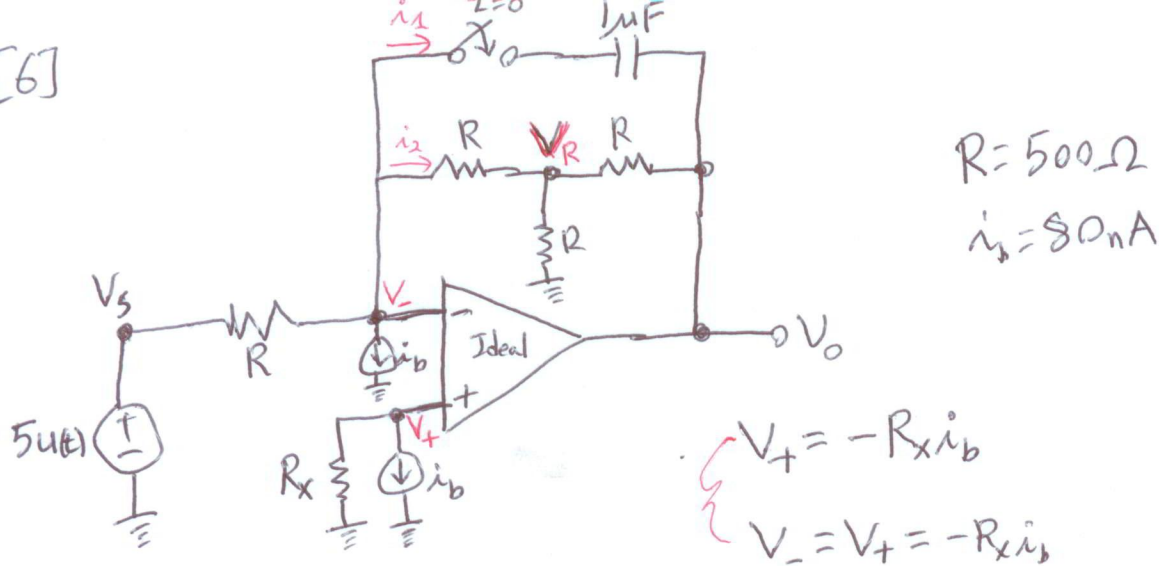

KCL at node  $V_-$ ;  $\boxed{\frac{V_s - V_-}{R} = i_b + i_1 + i_2} \dots \dots \dots (1)$

$\blacksquare i_1 = C \frac{d(V_- - V_o)}{dt} = -C \frac{d}{dt} (R_x i_b - V_o) = \boxed{-C \frac{dV_o}{dt}} (\because R_x i_b \text{ is constant})$

$\blacksquare i_2$  찾기;  $\frac{V_- - V_R}{R} = \frac{V_R}{R} + \frac{V_R - V_o}{R} = i_2$   
(KCL at node  $V_R$ )

$\Rightarrow V_R = V_- - i_2 R$

$\Rightarrow V_o = 2V_R - R i_2 = 2V_- - 3i_2 R = -2R_x i_b - 3i_2 R$

$\therefore i_2 = \boxed{-\frac{2R_x}{3R} i_b - \frac{V_o}{3R}}$

$\therefore i_1, i_2$ 를 식 (1)에 대입하면,

$V_s - V_- = R i_b - RC \frac{dV_o}{dt} - \frac{2}{3} R_x i_b - \frac{V_o}{3}$

$\therefore V_s = -RC \frac{dV_o}{dt} - \frac{V_o}{3} + R i_b - \frac{5}{3} R_x i_b$

Should be zero

~~$V_s = 5u(t)$~~   $V_o(t) = f(t)u(t)$  꼴을 만족시키기 위해서,

$R i_b - \frac{5}{3} R_x i_b = 0$

$\therefore R_x = \frac{3}{5} R = 300\Omega$

한편,  $V_s = 5u(t) = -RC \frac{dV_o}{dt} - \frac{V_o}{3}$ ,  $V_o(0) = 0V$  이므로,

$\Rightarrow V_o(t) = 15(e^{-\frac{t}{3RC}} - 1)u(t)$

$\therefore f(t) = 15(e^{-\frac{2000t}{3}} - 1)$