

Introduction to Verilog

Suheon Bae (suheon.bae@snu.ac.kr)

Hunjun Lee (hunjunlee7515@snu.ac.kr)

Dongup Kwon (dongup@snu.ac.kr)

High Performance Computer System (HPCS) Lab.

Mar. 13, 2018

Project

- In this project, you will design and implement an **in-order pipelined CPU** using Verilog.
- Tools
 - Hardware description language (HDL): Verilog
 - Design & simulation tool: Xilinx Vivado Design Suite


Overview

- In this project, you will learn **how to describe digital circuits in Verilog** and **how to use design tools** (*e.g., Vivado Design Suite*).
- All the assignments are related; that is, you need to complete all previous steps to do next assignment.
- Your assignment for this week is implementing a simple 16-bit ALU. This will also be used in the making of a CPU.
- **Goals**
 - Understand how to describe digital circuits in Verilog
 - Implement an ALU (i.e., a basic functional unit in CPUs)

Hardware Description Language (HDL)


HDL and Verilog

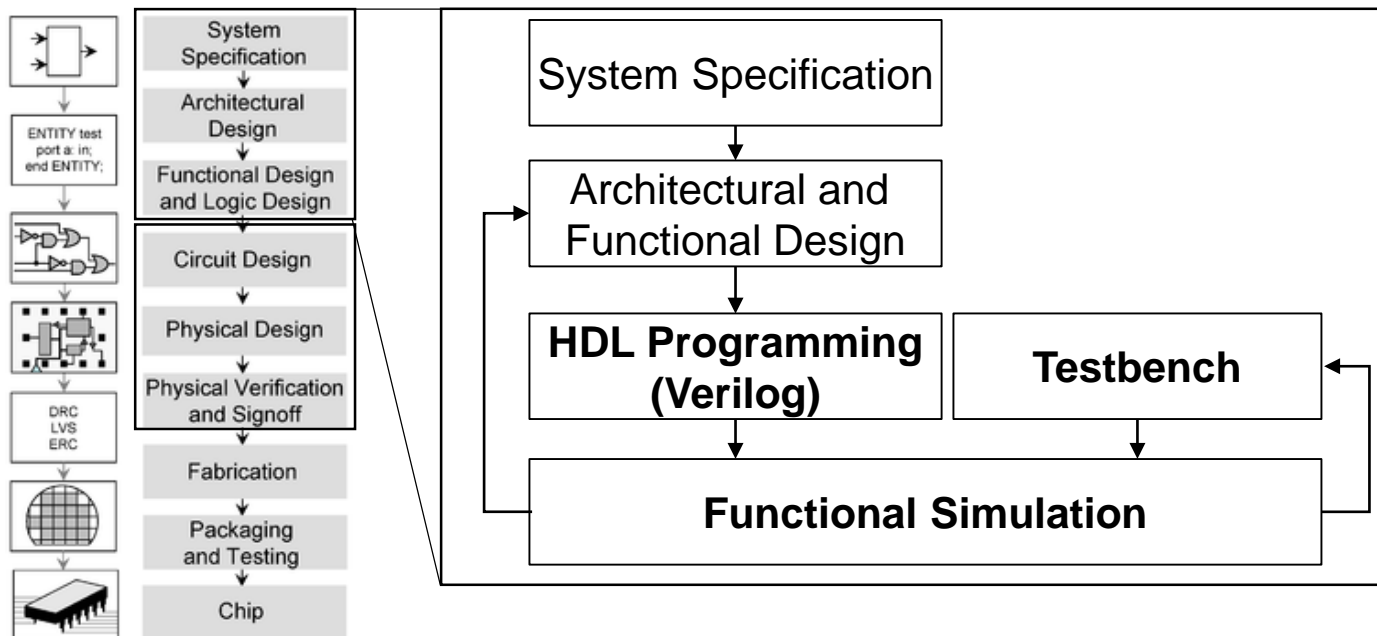- **HDL:** A formal notation designed to describe *electronic circuits*
- **Verilog:** Most widely used and well-supported HDL




Verilog Programming

How to describe a digital circuit?

 

What's inside a module?

Module A

 

Two-input AND gate

```
`timescale 1ns / 100ps
```

```
module AND (  
    input [3:0] A,  
    input [3:0] B,  
    output [3:0] Q  
);
```

```
    reg [3:0] Q;
```

```
    always begin  
        Q = A & B;
```

```
    end
```

```
endmodule
```

Source code

- Timescale

- Module

- Ports
- Data types
- Operators
- Behavior models
 - Assignments
 - If/case/loop statements
 - Timing / event control
 - Structured procedures

Structure

Timescale

- **`timescale** time_unit / time_precision
 - Example: **`timescale** 1 ns / 100 ps
- **time_unit**: the unit of measurement
 - Example: #100 = 100 * 1ns delay
- **time_precision**: the unit of simulation
- time_precision cannot specify a longer unit of time than time_unit.


Module

- A unit of hierarchical hardware structure
 - High-level modules create the instances of low-level modules and communicate with them through ports.
 - A **top-level** *module* is the highest-level module.
- Interfaces + behavior models

```
module AND (a, b, c);  
    input a;  
    input b;  
    output c;  
    assign c = a & b;  
endmodule
```

Interfaces (ports)

Behavioral models

 

Two-input AND gate

```
`timescale 1ns / 100ps
```

```
module AND (  
    input [3:0] A,  
    input [3:0] B,  
    output [3:0] Q  
);
```

```
    reg [3:0] Q;
```

```
    always begin  
        Q = A & B;
```

```
    end
```

```
endmodule
```

Source code

- ~~Timescale~~

- Module

- Ports
- Data types
- Operators
- Behavior models
 - Assignments
 - If/case/loop statements
 - Timing / event control
 - Structured procedures

Structure

Port

- A means of interconnecting modules
 - Optional, but usually necessary
- Port declaration: **input**, **output**, **inout** (bidirectional)

```
module AND (  
    input a,  
    input b,  
    output c  
);  
    assign c = a & b;  
endmodule
```

Data Type

- Data types is designed to represent the data storage and transmission elements.
- Values
 - **0**: a logic zero
 - **1**: a logic one
 - **x**: an unknown logic value
 - **z**: a high-impedance state
- **net** and **variable** data-type groups
 - **net**: a representation of physical connections (e.g., **wire**)
 - **variable**: an abstraction of data storage elements (e.g., **reg**)
- We will use only **wire** and **reg** data types

Data Type - Wire

- It defines a physical connection with a continuous assignment.
 - **wire** data type is the most representative.
- Example
 - wire [7:0] c;**
 - assign c = a & b;**
 - Then **c** is “physically connected” to the result of the “AND gate”.
 - **wire** data type usually describes a combinational circuit.

Data Type - Reg

- It is an abstraction of “storage elements” which can be read and written.
 - **reg** data type is the most representative. We use only this.
- Example
 - reg [7:0] c;**
 - always c = a & b;**
 - It is mainly used in a sequential circuit.

Syntax

- Comments : `//` or `/* */` (Similar to C language)
- Identifier : `[a-zA-Z_]([a-zA-Z0-9_$])+` (Up to 10 24 chars)
- Integer number : `<size>'<radix><value>`
 - `<size>` : # of bits
 - `<radix>` : h(hex), d(decimal), o(octal), b(binary)
 - `<value>` : Depend on the radix
 - X : “Unknown”, Z : “High Impedance”, _ : (Ignored)
 - Example: `8'b0`, `16'd7`, `32'hFF`

Two-input AND gate

```
`timescale 1ns / 100ps
```

```
module AND (  
    input [3:0] A,  
    input [3:0] B,  
    output [3:0] Q  
);
```

```
    reg [3:0] Q;
```

```
    always begin  
        Q = A & B;
```

```
    end
```

```
endmodule
```

Source code

- ~~Timescale~~

- Module

- ~~Ports~~

- ~~Data types~~

- Operators

- Behavior models

- Assignments

- If/case/loop statements

- Timing / event control

- Structured procedures

Structure

Operators

- Arithmetic
 - Binary : +, -, *, /, %
 - Unary : +, -
- Relational
 - Binary : <, >, <=, >=
- Equality
 - Binary : ==, !=
 - (comparing include x & z)
 - Binary : ==, !=
 - (returns x if a operand has x or z)
- Logical
 - Unary : !
 - Binary : &&, ||
- Bit-wise
 - Unary : ~
 - Binary : &, |, ^, ~^
- Reduction
 - Unary : &, ~&, |, ~|, ^, ~^
- Shift
 - Binary : <<, >>
- Concatenation
 - {a, b, c, ...}
- Replication
 - {n, {m}}
- Conditional
 - a?b:c

Addressing

- Vector bit-select and part-select addressing
 - **Examples**
 - `reg [63:0] word;`
 - `word[0]`
 - `word[7:0]`
 - `word[0+:8] // == word[7:0]`
 - `word[15-:8] // == word[15:8]`
 - `word[x] // == x (unknown value)`
 - `word[64] // == x (unknown value)`

Addressing

- Vector bit-select and part-select addressing
 - **Examples**
 - `reg [7:0] mem[1023:0];`
 - `mem[0]` // access the first element
 - `mem[0][3:0]` // access lower 4 bits of word
 - `mem[3:0]` // Illegal

Two-input AND gate

```
`timescale 1ns / 100ps
```

```
module AND (  
    input [3:0] A,  
    input [3:0] B,  
    output [3:0] Q  
);
```

```
    reg [3:0] Q;
```

```
    always begin  
        Q = A & B;
```

```
    end
```

```
endmodule
```

Source code

- ~~Timescale~~

- Module

- ~~Ports~~

- ~~Data types~~

- ~~Operators~~

- Behavior models

- Assignments

- If/case/loop statements

- Timing / event control

- Structured procedures


Structure

Behavioral Model

- Continuous assignment
- Procedural assignment
- if statement
- Case statement
- Loop statement
- Timing controls
- Structured procedures

Continuous Assignment

 - It drives values onto **wire** or defines a connection for **wire**.
 - **wire** c;
 - **assign** c = a & b; // the type of c should be the net.
- With a declaration of wire
 - **wire** c = a & b;



Procedural Assignments

- It puts values in **reg**, and **reg** holds the value until the next procedural assignment to that variable.
- It occurs within procedures such as **always** and **initial**.
 - **reg** x;
 - **always** x = 1; // the data type of x should be **reg**.
 - **wire** x;
 - **always** x = 1; //this kind of assignment to wire type will incur **error!! Do not do this!!!!**

Non-blocking & Blocking Assignment

- The two mechanism of *procedural assignments*
- It is really important but confusing, so you have to understand it very well.

Blocking assignment (=)

- It defines the execution order of statements.
- **Examples**
 - `reg a, b;`
 - `always begin`
 - `a = 0;`
 - `b = 0;`
 - `end`

Non-blocking assignment (<=)


- It doesn't specify the execution order of statements.
- Assignments within the same time step can be made without regard to order or dependence upon each other.
- **Examples**
 - `reg a, b;`
 - `always begin`
 - `a <= 0;`
 - `b <= 0;`
 - `end`

Blocking vs. Non-blocking

```
module example ();  
  reg a, b, c;  
  initial begin  
    b << a;  
    c << b;  
  end  
endmodule
```


<< is blocking (=)

	a	b	c
Before	0	1	x
After	0	0	0

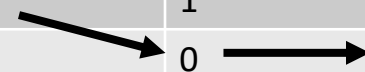

<< is non-blocking (<=)

Cycle	a	b	c
Before	0	1	x
After	0	0	1



Mixing Blocking & Non-blocking

- Don't even think about mixing them inside a module
- There is no syntactic error, but it is hard to predict the consequence.
- **reg** – procedural assignment
 - Edge-sensitive storage elements – non-blocking assignment (ex D flip flops ..)
 - Combinational logics – blocking assignment (ex ALU ..)

Two-input AND gate

```
`timescale 1ns / 100ps
```

```
module AND (  
    input [3:0] A,  
    input [3:0] B,  
    output [3:0] Q  
);
```

```
    reg [3:0] Q;
```

```
    always begin  
        Q = A & B;
```

```
    end
```

```
endmodule
```

Source code

- ~~Timescale~~

- Module

- ~~Ports~~

- ~~Data types~~

- ~~Operators~~

- Behavior models

- ~~Assignments~~

- If/case/loop statements

- Timing / event control

- Structured procedures

Structure

If statement

- It executes a statement conditionally.

```
module example ();  
    // ...  
    initial begin  
        if (a == 5) begin  
            b = 15;  
        end  
        else begin  
            b = 25;  
        end  
    end  
endmodule
```


Case statement

- It executes a statement conditionally.

```
module example ();  
  // ...  
  initial begin  
    case (a)  
      5: b = 15;  
      default: b = 25;  
    endcase  
  end  
endmodule
```

Loop statement - repeat

```
module example ();  
    // ...  
    initial begin  
        repeat (4) c = c + 1;  
    end  
endmodule
```

≡

```
module example ();  
    // ...  
    initial begin  
        c = c + 1;  
        c = c + 1;  
        c = c + 1;  
        c = c + 1;  
    end  
endmodule
```

Loop statement - forever

- Same as repeat (∞)

```
module example ();  
    // ...  
    initial begin  
        forever c = c + 1;  
    end  
endmodule
```

≡

```
module example ();  
    // ...  
    initial begin  
        c = c + 1;  
        c = c + 1;  
        c = c + 1;  
        // infinitely repeated  
    end  
endmodule
```

Loop statement – while, for

- It describes a repetition task, but sometime it cannot be implemented as a real circuit.
- The typical usage is an array initialization.

```
module example ();  
    initial begin  
        while (c < 10)  
            c = c + 1;  
  
    end  
endmodule
```

```
module example ();  
    initial begin  
        for (c=0; c<10; c++)  
            // ...  
  
    end  
endmodule
```

Two-input AND gate

```
`timescale 1ns / 100ps
```

```
module AND (  
    input [3:0] A,  
    input [3:0] B,  
    output [3:0] Q  
);
```

```
    reg [3:0] Q;
```

```
    always begin  
        Q = A & B;
```

```
    end
```

```
endmodule
```

Source code

- ~~Timescale~~

- Module

- ~~Ports~~

- ~~Data types~~

- ~~Operators~~

- Behavior models

- ~~Assignments~~

- ~~If/case/loop statements~~

- Timing / event control

- Structured procedures

Structure

Timing Controls - Delay & Event

- *Delay* and *event* are two methods for specifying when the procedural assignments occurs.

Delay control

- Delay control
 - Delay a procedural statement in its execution
 - **Examples**
 - `#10 rega = reab;`
 - `#regr regr = regr + 1;`

Delay control

- It is used for describing the timing of real hardware, but not for controlling behaviors of Verilog code.
- So, you must not use “delay”, except for a clock signal and a testbench.

Event control

- Event control
 - Synchronize a procedural statement with a value change on a `wire` or `reg` or the occurrence of a declared event
 - **Examples**
 - `@r rega = reab;`
 - `@(posedge clock) rega = regb;`
 - `always @(negedge clock) rega = regb;`
 - `always @(a, b, c, d, e)`
 - `always @(posedge clk, negedge rstn)`
 - `always @(a or b, c, d or e)`

Event control

- Implicit event-expression list `@(*)`
 - Add all **wire** and **reg** that are read by the statements
 - **Examples**
 - `always @(*) begin // equivalent to @(a or b or c or d)`
 - `x = a ^ b;`
 - `@(*) // equivalent to @(c or d)`
 - `x = c ^ d;`
 - `end`

Event control

- We can represent a complex **combinational circuit** with an event.

```
module example ();  
    wire a, b, c;  
    assign c = ~(a & b);  
endmodule
```

≡

```
module example ();  
    wire a, b;  
    reg c;  
    always @(a or b) begin  
        c = ~(a & b);  
    end  
endmodule
```

Event control

- How to describe edge-storage elements
 - Non-blocking assignments and `posedge` events
 - **Examples**
 - `always @(posedge clk) begin`
 - `ff1 <= ff1_next;`
 - `ff2 <= ff2_next;`
 - `...`
 - `end`
- Can be used to design **sequential circuit**

Two-input AND gate

```
`timescale 1ns / 100ps
```

```
module AND (  
    input [3:0] A,  
    input [3:0] B,  
    output [3:0] Q  
);
```

```
    reg [3:0] Q;
```

```
    always begin  
        Q = A & B;
```

```
    end  
endmodule
```

Source code

- ~~Timescale~~

- Module

- ~~Ports~~

- ~~Data types~~

- ~~Operators~~

- Behavior models

- ~~Assignments~~

- ~~If/case/loop statements~~

- ~~Timing / event control~~

- Structured procedures

Structure

Structured Procedures

- **always, initial**
- They are necessary for designing sequential circuit.

Structured Procedures - initial

- It is executed once at the beginning.

```
module example ();  
    reg clk, x;  
    initial clk <= 0;  
    initial x <= 1;  
endmodule
```

≡

```
module example ();  
    reg clk, x;  
    initial begin  
        clk <= 0;  
        x <= 1  
    end  
endmodule
```

- It initializes reg clk and x.
- It can involve multiple statements with begin ... end.

Structured Procedures - always

- **always** is equal to the infinite repetition of a initial block.

```
module example ();  
    reg clk;  
    initial clk <= 0;  
    initial begin  
        #50 clk <= ~clk;  
        #50 clk <= ~clk;  
        #50 clk <= ~clk;  
        // infinitely repeated  
    end  
endmodule
```

≡

```
module example ();  
    reg clk;  
    initial clk <= 0;  
    always begin  
        #50 clk <= ~clk;  
    end  
endmodule
```


Some more advanced / additional stuffs
from now on

Overview

- **Compiler directives**

- ~~`timescale,~~ **`include, `define**

- **Data types**

- ~~wire, reg,~~ **arrays, parameters**

- **Expressions**

- ~~Operators, operands~~

- **Assignments**

- ~~Continuous assignments, procedural assignments, blocking/non-blocking assignment (procedural)~~

- **Behavioral modeling**

- ~~Structured procedures, conditional statement (if-else), case statement, looping statements~~
- ~~Timing control, event control, event-expression list~~

- **Hierarchical structures**

- ~~Modules, ports,~~ **port connection**

Compiler directives (1)

- Control the compilation of a Verilog description
 - All Verilog compiler directives are preceded by the (```) grave accent mark.
 - It is recommended that they appear outside a module declaration.
- **``timescale`**
 - Specify the time unit and time precision
 - **``timescale`** `time_unit` / `time_precision`

Compiler directives (2)

- **``include`**
 - Insert the entire contents of a source file in another file during compilation
 - ``include filename`
- **``define`**
 - Represent commonly used pieces of text
 - ``define macro_name macro_text`
 - **Examples**
 - ``define wordsize 8`
 - `reg [`wordsize-1:0] data;`

Compiler directives (3)

- **``define`**
 - ``define macro_name macro_text`
 - **More examples**
 - ``define first_half "start of string`
 - `$display(`first_half end of string");`
 - ``define max(a,b) ((a) > (b) ? (a) : (b))`
 - `n = `max(p+q, r+s);`

Overview

- **Compiler directives**

- ~~`timescale,~~ **`include,** **`define**

- **Data types**

- ~~wire, reg,~~ **arrays, parameters**

- **Expressions**

- ~~Operators, operands~~

- **Assignments**

- ~~Continuous assignments, procedural assignments, blocking/non-blocking assignment (procedural)~~

- **Behavioral modeling**

- ~~Structured procedures, conditional statement (if-else), case statement, looping statements~~
 - ~~Timing control, event control, event-expression list~~

- **Hierarchical structures**

- ~~Modules, ports,~~ **port connection**

Data types (1)

- Arrays
 - Group elements of the declared element type into multidimensional objects
- Memories – a one-dimensional array with elements of type **reg**
- **Examples**
 - **reg** [7:0] mem[255:0];
 - **reg** arrayA[7:0][255:0];
 - **reg** [7:0] regA \neq **reg** mem[7:0]

Data types (2)

- Assignment to array elements
- **More examples**
 - `reg [7:0] mem[255:0];`
 - `mem = 0; // Illegal syntax - attempt to write entire array`
 - `mem[1] = 0; // Assigns 0 to the second element of mem`

Data types (3)

- Module parameters (**parameter**)
 - Constant values – cannot be modified at run time
 - Can be modified at compilation time to have values that are different from those specified in the declaration assignment → module customization
 - **Examples**
 - `parameter msb = 7;`
 - `Parameter [3:0] mux_selector = 0;`
- Local parameters (**localparam**)
 - Cannot directly be modified by **defparam** or module instance parameter value assignments

Data types (4)

- **Parameter & localparam**

- **Examples**

- `module my_mem (addr, data);`
 - `parameter addr_width = 16;`
 - `parameter data_width = 8;`
 - `localparam mem_size = 1 << addr_width;`
 - `...`
 - `endmodule`
 - `module top;`
 - `...`
 - `my_mem #(12, 16) m(addr, data);`
 - `endmodule`

Overview

- **Compiler directives**

- ~~`timescale, `include, `define~~

- **Data types**

- ~~wire, reg, arrays, parameters~~

- **Expressions**

- ~~Operators, operands~~

- **Assignments**

- ~~Continuous assignments, procedural assignments, blocking/non-blocking assignment (procedural)~~

- **Behavioral modeling**

- ~~Structured procedures, conditional statement (if-else), case statement, looping statements~~
- ~~Timing control, event control, event-expression list~~

- **Hierarchical structures**

- ~~Modules, ports, port connection~~

Hierarchical structures (1)

- Module: a unit of hierarchical hardware structure
 - A top-level module is the highest-level module.
 - Interfaces + behavior models
- Module instantiation
 - **Examples**
 - `module ffnand (q, qbar, preset, clear);`
 - `output q, qbar;`
 - `input preset, clear;`
 - `endmodule`

 - `// Higher level module`
 - `ffnand ff (out1, out2, in1, in2);`

Hierarchical structures (2)

- Parameter value assignment by ordered list

- **Examples**

- **module** my_mem (addr, data);
 - **parameter** addr_width = 16;
 - **localparam** mem_size = 1 << addr_width;
 - **parameter** data_width = 8;
 - ...
 - **endmodule**
 - **module** top;
 - ...
 - my_mem #(12, 16) m(addr, data);
 - **endmodule**

Hierarchical structures (3)

- Connecting module instance ports by ordered list

- **Examples**

- `module topmod;`
- `wire [4:0] v;`
- `wire a,b,c,w;`
- `modB b1 (v[0], v[3], w, v[4]);`
- `endmodule`

- `module modB (wa, wb, c, d);`
- `inout wa, wb;`
- `input c, d;`
- `...`
- `endmodule`

Hierarchical structures (4)

- Connecting module instance ports by name

- **Examples**

- `module topmod;`
 - `wire [4:0] v;`
 - `wire a,b,c,w;`
 - `modB b1 (.wb(v[3]),.wa(v[0]),.d(v[4]),.c(w));`
 - `endmodule`

 - `module modB(wa, wb, c, d);`
 - `inout wa, wb;`
 - `input c, d;`
 - `...`
 - `endmodule`

Now some more practical tips

How to design digital circuit?

- Combinational circuit
 - Computation without memory elements
 - Continuous assignment
 - Blocking assignment
- Sequential circuit
 - Think of it as combinational circuit + memory
 - Non-blocking assignment

Combinational circuit -1

- Continuous assignment

```
`timescale 1ns / 100ps

module AND (
    input [3:0] A,
    input [3:0] B,
    output [3:0] Q
);

    assign Q = A & B

endmodule
```

Combinational circuit -2

- Blocking assignment

```
`timescale 1ns / 100ps
```

```
module AND (  
    input [3:0] A,  
    input [3:0] B,  
    output [3:0] Q  
);
```

```
    reg [3:0] Q;
```

```
    always begin  
        Q = A & B;  
    end
```

```
endmodule
```

Sequential circuit

- Non blocking assignment

```
`timescale 1ns / 100ps

module Dflipflop (
    input [3:0] A_in,
    input clk,
    output [3:0] A_out
);

    reg [3:0] A_out;

    always @(posedge clk)begin
        A_out <= A_in;
    end
endmodule
```

Assignment

- There will be assignment due next week
 - March, 20th
- You'll make 16bit ALU for your CPU
- You'll learn how to implement combinational logic in Verilog
- Detailed description of the project is uploaded in etl

Reference

- IEEE Standard for Verilog Hardware Description Language, IEEE Computer Society