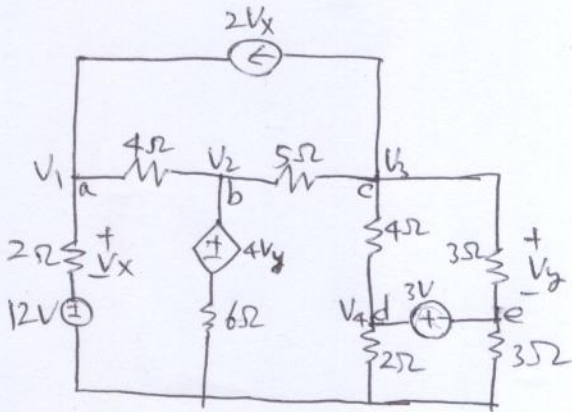


[17]



$$V_x = V_1 - 12$$

$$V_y = V_3 - (V_4 - 3)$$

Applying KCL,

$$\text{Node a: } \frac{V_1 - 12}{2} + \frac{V_1 - V_2}{4} - 2V_x = 0$$

$$\text{Node b: } \frac{V_2 - V_1}{4} + \frac{V_2 - V_3}{5} + \frac{V_2 - 4V_y}{6} = 0$$

$$\text{Node c: } 2V_x + \frac{V_3 - V_2}{5} + \frac{V_3 - V_4}{4} + \frac{V_y}{3} = 0$$

$$\text{Supernode d-e: } \frac{V_4 - V_3}{4} + \frac{V_4}{2} + \frac{V_4 - 3}{3} + \frac{V_4 - 3 - V_3}{3} = 0$$

$$\Rightarrow V_1 = \frac{693}{26} \text{ V}$$

$$V_2 = -\frac{1593}{26} \text{ V}$$

$$V_3 = -\frac{999}{13} \text{ V}$$


$$V_4 = -\frac{393}{13} \text{ V}$$

[2] (a) Applying KCL,

$$\text{node a: } \frac{V_1 - 22}{2.2} + \frac{V_1 + 12}{5.6} + \frac{V_1 - V_2}{3.3} = 0$$

$$\text{node b: } \frac{V_2 - 6}{6.8} + \frac{V_2 - V_1}{3.3} + \frac{V_2 - V_{\text{test}}}{1.2} = 0$$
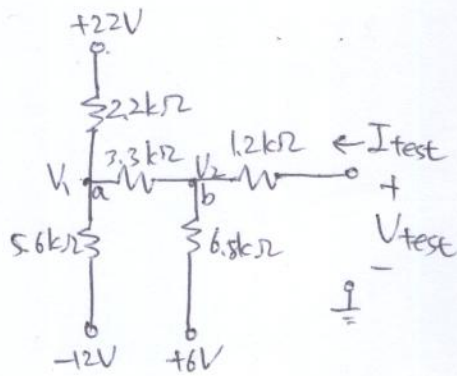
$$I_{\text{test}} = \frac{V_{\text{test}} - V_2}{1.2}$$




$V_1, V_2$ 를 소거하여 정리하면,

$$I_{\text{test}} = \frac{V_{\text{test}} - \frac{3510936}{360956}}{\frac{18222336}{4509450}}$$


$$\therefore V_t = \frac{3510936}{360956} \approx 9.732 \text{ V}$$

$$R_{\text{th}} = \frac{18222336}{4509450} \approx 4.041 \text{ k}\Omega$$

등가 회로:

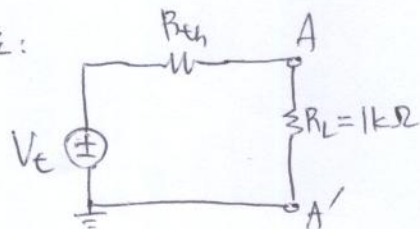

(b) 등가 회로:

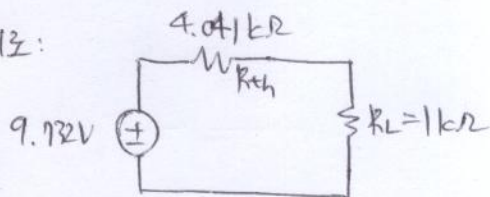

$R_{\text{th}}$ 가 소모하는 전력,

$$P_{R_{\text{th}}} = i^2 R_{\text{th}}$$


$$= \left( \frac{9.732}{(4.041 + 1) \times 1000} \right)^2 \cdot 4.041 \times 1000 \text{ [W]}$$

$$\approx 15.06 \text{ mW}$$

(c). Applying KCL,

$$\frac{V_1 - 22}{2.2} + \frac{V_1 + 12}{5.6} + \frac{V_1 - V_2}{3.3} = 0.$$
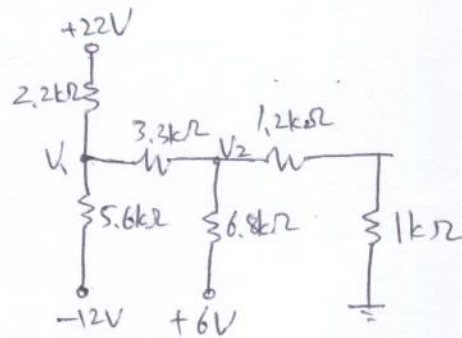
$$\frac{V_2 - V_1}{3.3} + \frac{V_2 - 6}{6.8} + \frac{V_2}{2.2} = 0.$$



$$\Rightarrow V_1 = \frac{17588145848}{1797914437} \approx 9.771 \text{ V}$$

$$V_2 = \frac{64367160}{15116464} \approx 4.258 \text{ V}.$$

$$P = P_{2.2k\Omega} + P_{3.3k\Omega} + P_{5.6k\Omega} + P_{6.8k\Omega} + P_{1.2k\Omega}$$

$$= \frac{(9.771 - 22)^2}{2.2} + \frac{(9.771 + 12)^2}{5.6} + \frac{(9.771 - 4.258)^2}{3.3} + \frac{(4.258 - 6)^2}{6.8} + \frac{\left(\frac{1.2}{2.2} \cdot 4.258\right)^2}{1.2}$$

$$\doteq 67.98 + 9.21 + 84.64 + 0.45 + 4.49$$

$$\doteq 166.76 \text{ [mW]}$$



[3] (a) 회로망의 방정식 세우기

$$V_b = V_x$$

$$\textcircled{1} \frac{V_a - V_b}{3} + \frac{V_a - V_c}{2} + \frac{V_a - 3V_x}{2} + \frac{V_a - 3V_x - (V_c - 10)}{4} = 0 \quad \left. \vphantom{\frac{V_a - V_b}{3}} \right] \rightarrow \text{supernode}$$

$$\textcircled{2} \frac{V_c - V_a}{2} + \frac{V_c - V_b}{1} + \frac{V_c - 10 - (V_a - 3V_b)}{4} - 6 = 0$$

$$\textcircled{3} \frac{V_b - V_a}{3} + \frac{V_b - V_c}{1} + \frac{V_b}{1} = 0$$

각 식당 2점  $\times 3 = 6$ 점

(b) 전압  $V_a, V_b, V_c$

$$\textcircled{1} \times 12 \rightarrow 12V_a - 36V_b - 12V_c = -30$$

$$\textcircled{2} \times 4 \rightarrow -3V_a - V_b + 7V_c = 34$$

$$\textcircled{3} \times 3 \rightarrow -V_a + 7V_b - 3V_c = 0$$


$$\begin{bmatrix} 12 & -36 & -12 \\ -3 & -1 & 7 \\ -1 & 7 & -3 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} -30 \\ 34 \\ 0 \end{bmatrix}$$

$$V_a = 21.8V \quad V_b = 9.8V \quad V_c = 15.6V$$

각 전압당 3점. 단위 안쓰면 1점씩 감점.

(a)의 회로망의 방정식을 잘못 세워서 전압값이 틀리면 1점

(c)  $V_a$ 에서 아래로 향하는 전류:  $I_{DS}$

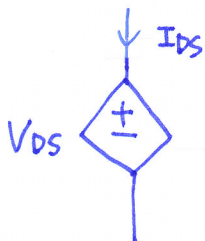

$$\frac{V_a - V_c}{2} + I_{DS} + \frac{V_a - V_b}{3} = 0$$


$$I_{DS} = -\frac{V_a - V_c}{2} - \frac{V_a - V_b}{3} = -7.1A \rightarrow 2\text{점 (식은 맞는데 계산이 틀리면 1점 감점)}$$

$$P = -V_{DS} \cdot I_{DS} = -(3V_b)(-7.1) = 21.3V_b = 208.74W \rightarrow 5\text{점}$$

부호 틀리면 2점 감점

$V_{DS} = 3V_b$ 가 위에서 틀린 경우 1점 감점

[4] a)  $V_{oc}$  [7점]

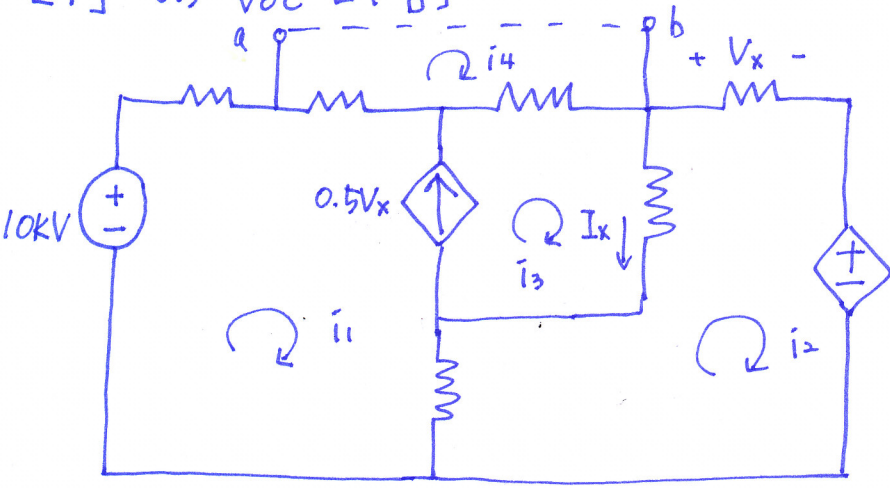

equivalent circuit  
using source transformation

(all of  $R : 1k\Omega$ )

$$I_x = i_3 - i_2$$

$$V_x = 1000 i_2$$

loop 1 (super mesh)

$$2000 \bar{i}_1 + 1000 \bar{i}_3 + 1000 (\bar{i}_3 - \bar{i}_2) + 1000 (\bar{i}_1 - \bar{i}_2) = 10^4$$

$$\Rightarrow 3\vec{i}_1 - 2\vec{i}_2 + 2\vec{i}_3 = 10 \quad \dots \textcircled{1}$$

loop 2

$$1000(i_2 - \bar{i}_1) + 1000(i_2 - \bar{i}_3) + 1000\bar{i}_2 + 0.1(i_3 - \bar{i}_2) = 0$$

$$\Rightarrow 10000 \bar{i}_1 - 29999 \bar{i}_2 + 9999 \bar{i}_3 = 0 \dots \textcircled{2}$$

$$\vec{I}_3 - \vec{I}_1 = 0.5 V_x = 500 \vec{i}_2 \Rightarrow \vec{I}_1 + 500 \vec{i}_2 - \vec{I}_3 = 0 \dots \textcircled{3}$$

solve (1)(2)(3)  $i_1 = 10.1657 \text{ A}$   $i_2 = -0.0409 \text{ A}$   $i_3 = -10.2894 \text{ A}$

$$V_{oc} = 1000 (i_1 + i_3) = -123.75 [V]$$

b)  $I_{sc}$  [7점]

$$3\bar{i}_1 - 2\bar{i}_2 + 2\bar{i}_3 - 2\bar{i}_4 = 10$$


$$10000\bar{i}_1 - 29999\bar{i}_2 + 9999\bar{i}_3 = 0$$

$$\bar{i}_1 + 500\bar{i}_2 - \bar{i}_3 = 0$$

$$\bar{i}_1 + \bar{i}_3 - 2\bar{i}_4 = 0$$

$$\text{solve } I_{sc} = -61 \text{ [mA]}$$

c) [6점]

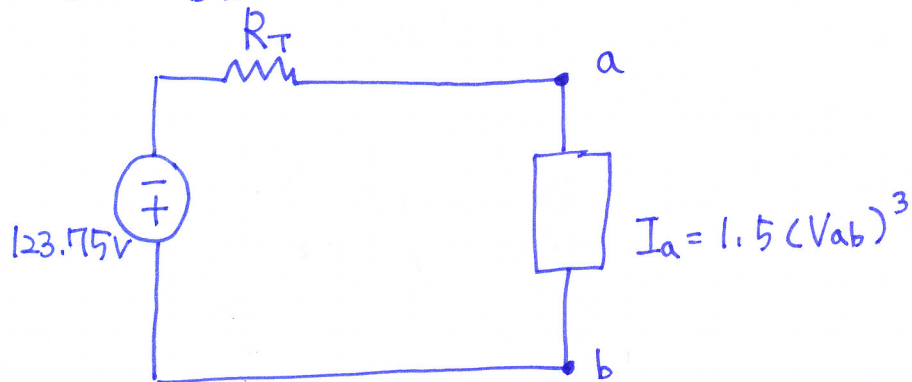

$$R_T = \frac{V_{oc}}{I_{sc}} = 2.0248 k\Omega$$

KCL on a


$$\frac{V_{ab} + 123.75}{2.0248 k\Omega} + 1.5(V_{ab})^3 = 0$$

$$V_{ab} = -334.18 \text{ mV}$$

$$I_a = -55.98 \text{ [mA]}$$

[5] - (1) (total 8pt)

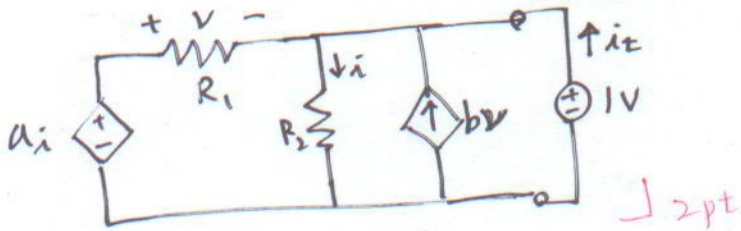$V_{oc} = V_{th} = 0V$  ( $\because$  No independent source) 1 pt




$i R_2 = 1V \Leftrightarrow i = \frac{1}{R_2}$

$V = ai - 1 = \frac{a}{R_2} - 1$

KCL;  $\frac{V}{R_1} + i_t + bv = i$

$\therefore i_t = \frac{1}{R_2} - b \left( \frac{a}{R_2} - 1 \right) - \frac{1}{R_1} \left( \frac{a}{R_2} - 1 \right)$

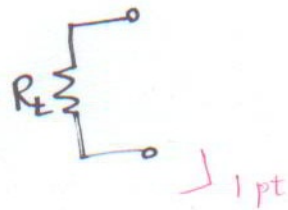
$\therefore R_t = \frac{1}{i_t} = \frac{1}{\frac{1}{R_2} - \frac{b(a-R_2)}{R_2} - \frac{(a/R_2-1)}{R_1}}$  1 pt, 3 pt.



(same result when 1A current source is used instead of 1V voltage source)




[5]-(2) (total 12pt)

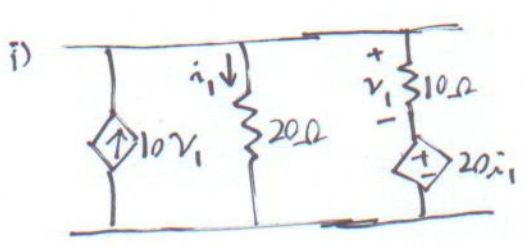


by using the result of [5]-(1),
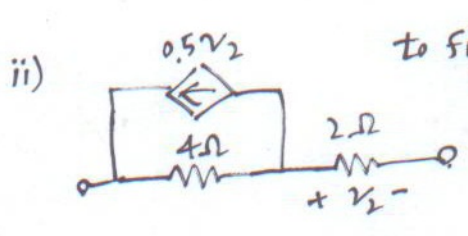
$$R_t = \frac{1}{\frac{1}{20} - \frac{-10(20/20-1)}{1} - \frac{(20/20-1)}{10}} = 20 \Omega$$



To find Thevenin equivalent resistor,

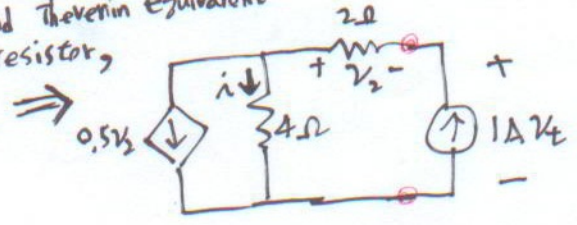


$$v_2 = -2V$$

$$i = 1A + 1A = 2A$$

$$\therefore v_t = 8V + 2V = 10V$$


As a result, The circuit can be simplified as following.
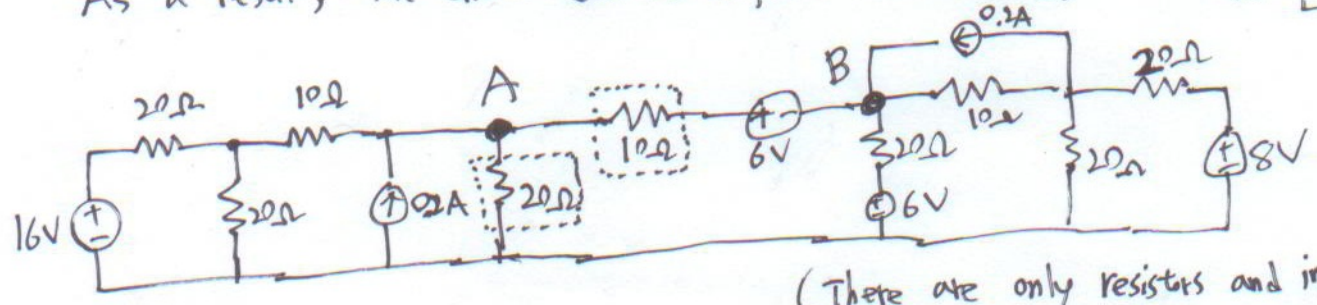
$$\therefore R_t = \frac{v_t}{i} = 10 \Omega$$




(There are only resistors and independent sources)

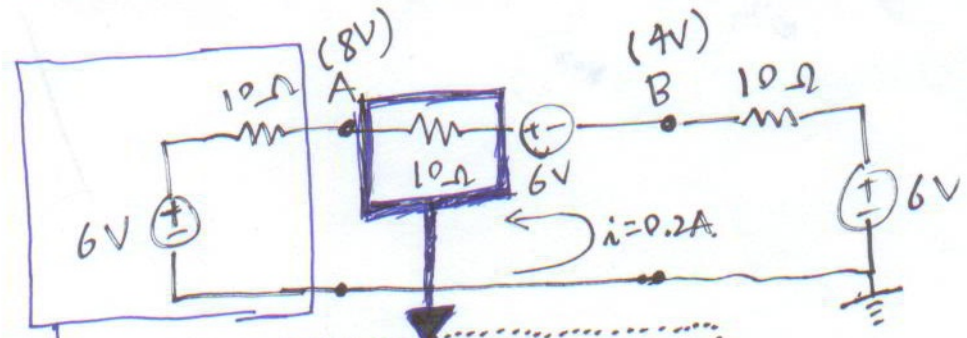Using Source Transformation, we can simplify the circuit into the following circuit.




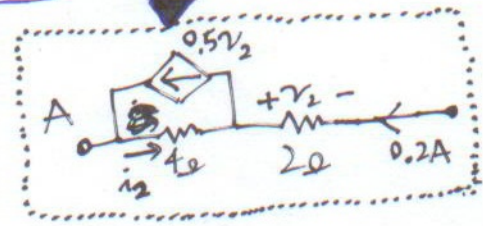
The current from node B to node A is 0.2A



$$v_2 = -0.4V$$

$$i_2 + 0.2 = 0.5v_2 = -0.2$$

$$\therefore i_2 = -0.4A$$

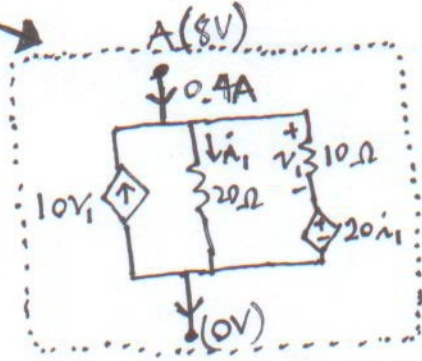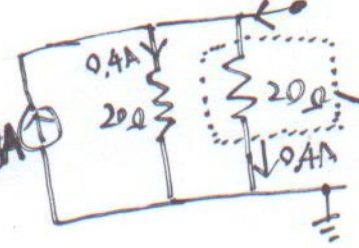


$$20i_1 = 8V$$

$$\therefore i_1 = 0.4A$$



[6] (a) (total 12pt)


Using Thevenin equivalent ckt,

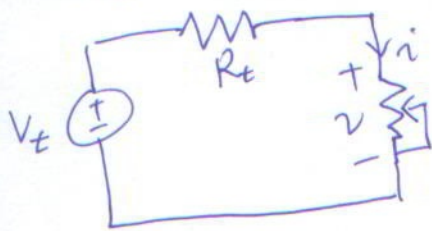

$$v = V_t - iR_t$$


$$\therefore V_t = 5V, R_t = 625\Omega$$

1pt                      1pt

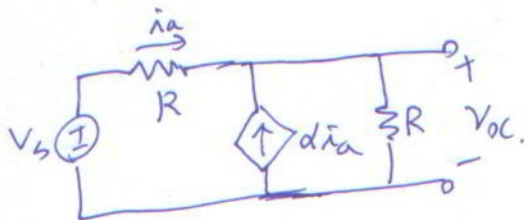

$$V_{oc} = V_t = R i_a (1+d) = R (1+d) \frac{(V_s - V_t)}{R} = (1+d)(V_s - V_t) \dots \textcircled{1}$$

2pt

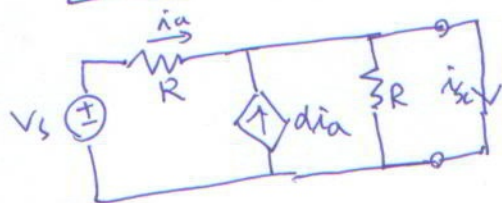

$$i_{sc} = (d+1)i_a = \frac{(d+1)V_s}{R}$$

$i_a = \frac{V_s}{R}$

$$R_t = \frac{V_t}{i_{sc}} = \frac{R V_t}{(d+1)V_s} \dots \textcircled{2}$$

2pt

Combining  $\textcircled{1}$  and  $\textcircled{2}$ ;

$$V_s = \frac{V_t R}{R - R_t} = \frac{5R}{R - 625}$$

1pt

$$d = \frac{5}{V_s - 5} - 1$$

1pt

for student A,  $R = 500\Omega$ ,

$$\begin{cases} V_s = -20V \\ d = -1.2 \text{ A/A} \end{cases}$$


1pt                      1pt

for student B,  $R = 1k\Omega$ ,

$$\begin{cases} V_s = 40/3 \text{ V} \\ d = -0.4 \text{ A/A} \end{cases}$$


1pt                      1pt

[6]-(b) (total 8pt)

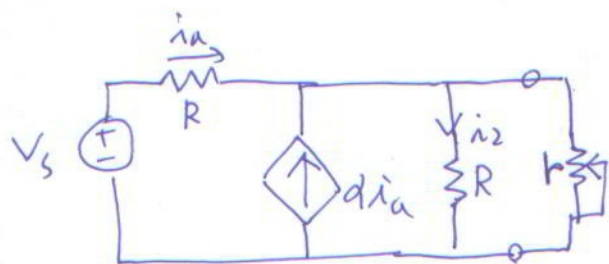

$r$  is variable resistor. ( $0 \leq r < \infty$ )

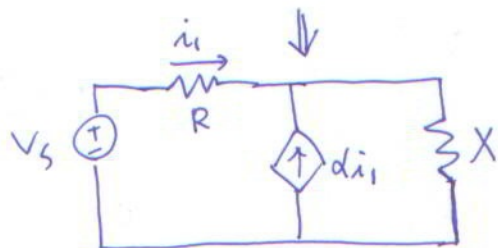Let  $R \parallel r = X$  ( $0 \leq X < R$ )



$$i_2 = (d+1)i_1 \frac{r}{R+r} = \frac{(d+1)i_1 X}{R}$$

$i_1$  and  $i_2$  must be located in the range of  $-15\text{mA}$  to  $15\text{mA}$


$$\star (i_1, i_2; -15\text{mA} \leq i_1 \leq 15\text{mA}, -15\text{mA} \leq i_2 \leq 15\text{mA})$$

KVL;  $-V_s + i_1 R + (d+1)i_1 X = 0$

$$\therefore i_1 = \frac{V_s}{(d+1)X + R}, \quad i_2 = \frac{(d+1)V_s X}{R[(d+1)X + R]} \quad (0 \leq X < R)$$

for student A,  $R = 500\Omega$ ,  $V_s = -20\text{V}$ ,  $d = -1.2$

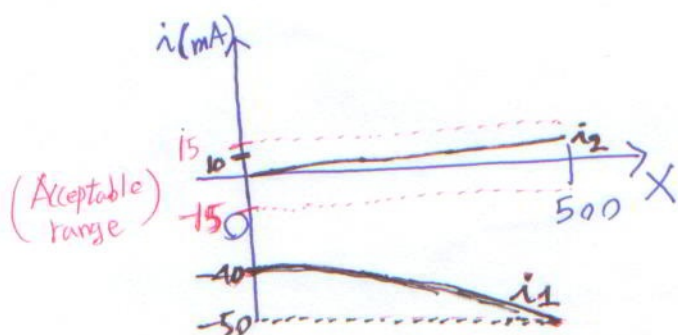
$$\therefore i_1 = \frac{-20}{-0.2X + 500} = \frac{100}{X - 2500}, \quad i_2 = \frac{-0.04X}{X - 2500} \quad (0 \leq X < 500)$$



$\Rightarrow$  Student A's circuit is not working properly because the current in the resistor exceeded acceptable range.

for student B,  $R = 1\text{k}\Omega$ ,  $V_s = 40/3\text{V}$ ,  $d = -0.4$
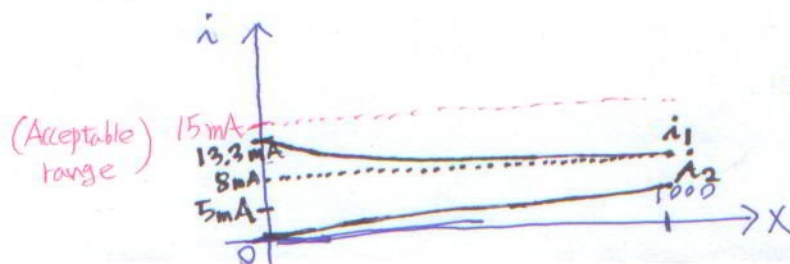
$$\therefore i_1 = \frac{40/3}{0.6X + 1000}, \quad i_2 = \frac{8X}{1000(0.6X + 1000)} \quad (0 \leq X < 1000)$$



$\Rightarrow$  Student B's circuit is working normally because the currents in the resistor do not exceed acceptable range.